

2011/12


# Cellular IC design – RF, Analog, Mixed-Mode

**Mohammed Abdulaziz, Mattias Andersson, Jonas Lindstrand,  
Xiaodong Liu, Anders Nejdell**

**Ping Lu, Luca Fanori**

 **Martin Anderson, Lars Sundström, Pietro Andreani**

Department for Electrical and Information Technology  
Lund University



# Overview

---

- A reconfigurable channel-select filter
  - Mohammed Abdulaziz
- A continuous-time  $\Delta\Sigma$  A/D converter
  - Xiaodong Liu
- A filtering continuous-time  $\Delta\Sigma$  A/D converter
  - Mattias Andersson
- PA / TX circuits
  - Jonas Lindstrand
- A noise-shaping time-to-digital converter
  - Ping Lu



## Overview – II

---


- Linear RX front-end (previous presentation)
  - Anders Nejdel (SSF DARE project)
- Highly efficient class-C VCO (next presentation)
  - Luca Fanori (FP7 DRAGON project, SoS)
- RX BB for carrier aggregation (not included)
  - Martin Anderson, Lars Sundström


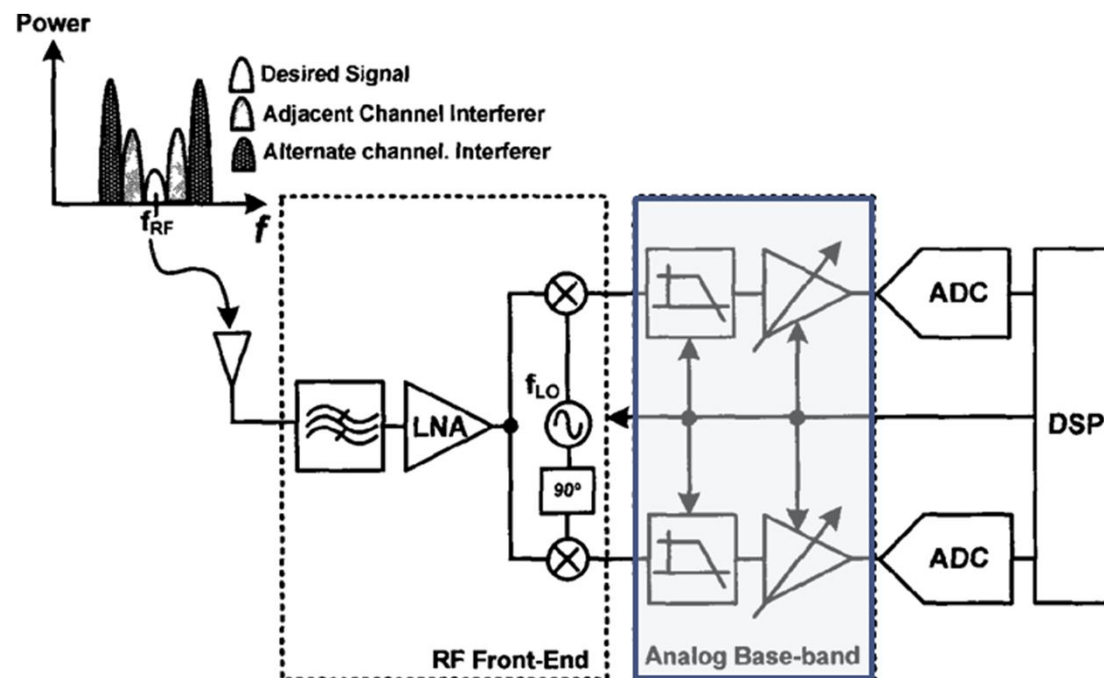
# A reconfigurable channel-select filter (SSF DARE project)


Mohammed Abdulaziz

- Limit unwanted signals falling close to the baseband
- Relax the dynamic range requirements of the ADC


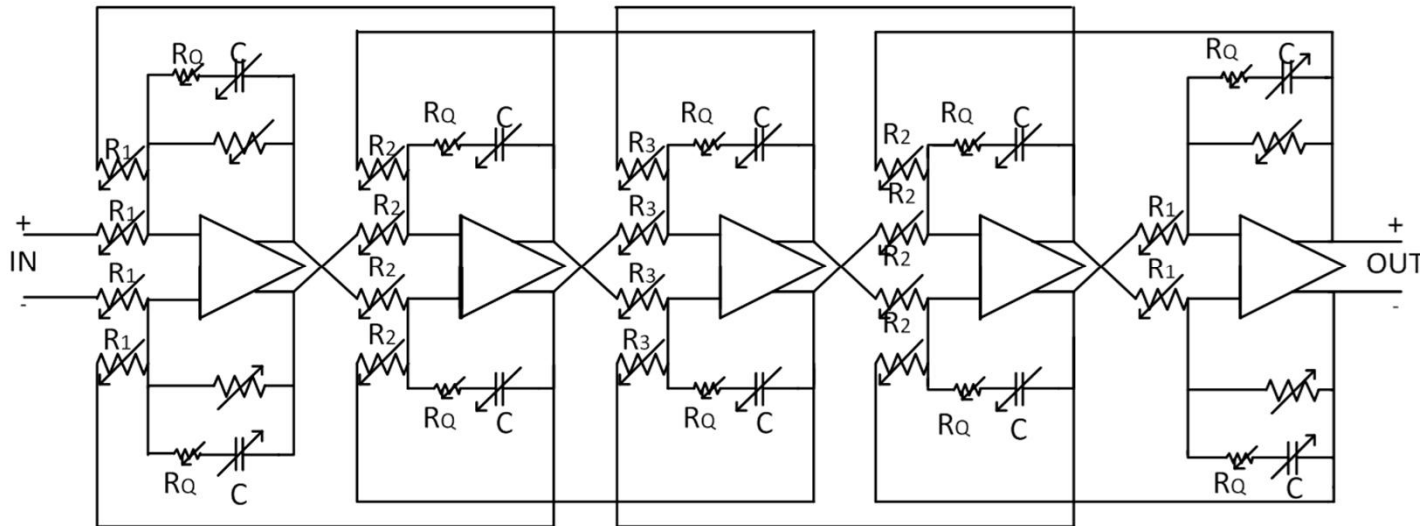
# Project goals and challenges

- Linearity vs. noise control via digital control word
- Break the linearity vs. noise trade-off with a linearization scheme



- R<sub>Q</sub>: tunes the Q factor of the filter
- C: selects the operating band
- R<sub>1</sub>, R<sub>2</sub> and R<sub>3</sub>: compensate process variations




# Chip photo and Simulations

---

Taped out in June 2012, under measurement

Parameter	Value
Process Technology	65nm CMOS
Response	Chebyshev
Order	5 <sup>th</sup>
Power Supply	1.2 V
Current Consumption	3.2 mA
Input Referred Noise	38nV/√Hz
IIP3	24 dBm
Frequency Bands	20/15/10/5/3/1.4 MHz
Tuning Range	±40%

 

Complete RF front-end (LNA+Mixer+Filter) for Oct. 2012 TO





# Wideband A/D converters (SSF DARE project)

Xiaodong Liu

- 3<sup>rd</sup> order, 4-bit,  $f_s=640\text{MHz}$ ,  $\text{BW}=20\text{MHz}$  ( $\text{OSR}=16$ )
- Goal
  - To meet the bandwidth requirement of LTE Advanced standard (20MHz to 100MHz)
  - To demonstrate the feasibility of reducing power consumption while maintaining a good SNR by means of digital enhancement techniques
- Approach
  - Continuous-time Delta-Sigma modulator is attractive for BW beyond 20MHz
  - Pipelined A/D is a good candidate for the LTE Advanced maximum bandwidth of 100MHz



# Delta-Sigma A/D – system level design

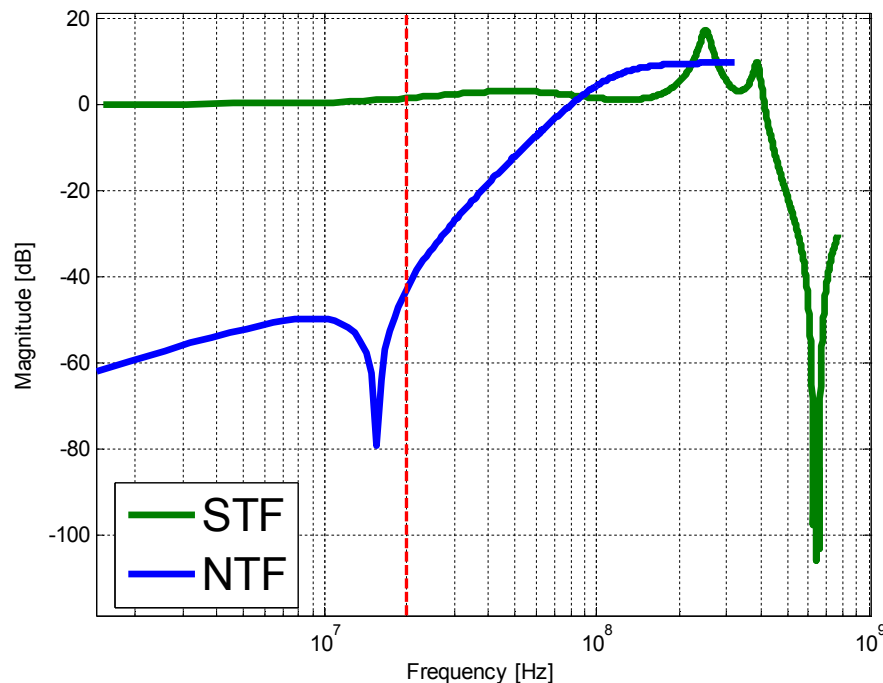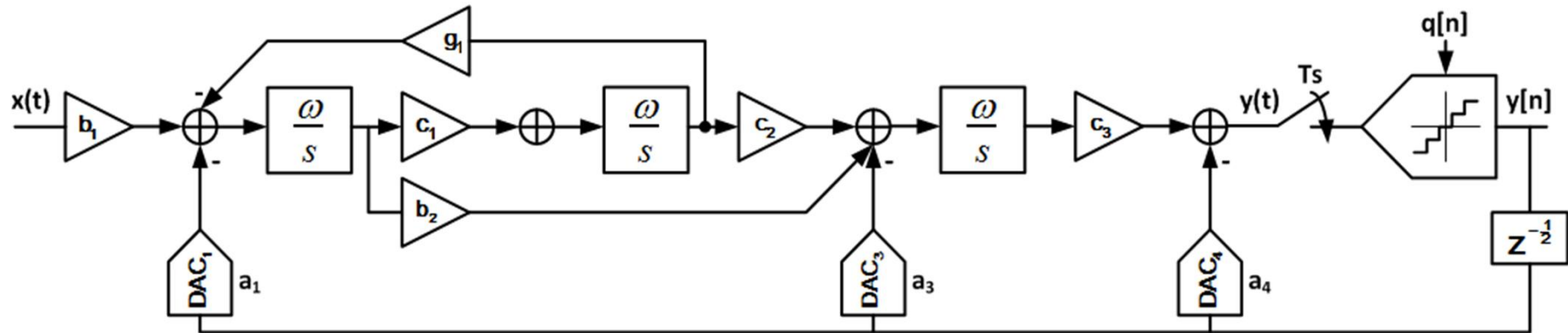


- CT sigma-delta modulator with inherent anti-aliasing
- Combination of feedforward and feedback topology
- Direct feedback path around quantizer through  $DAC_4$  for delay compensation




 
# Circuit implementation



- Active-RC op-amp filter with feedforward gm compensation in the op-amp
- Current-steering DAC with non-return to zero (NRZ) pulses
- Dynamic element matching to mitigate distortion effect of mismatch in the DAC elements
- TO in March 2013


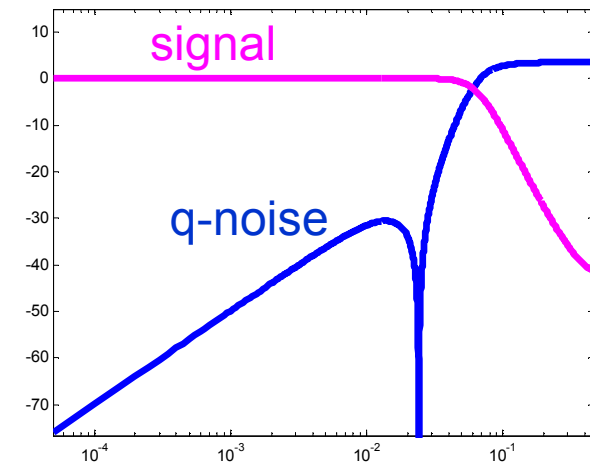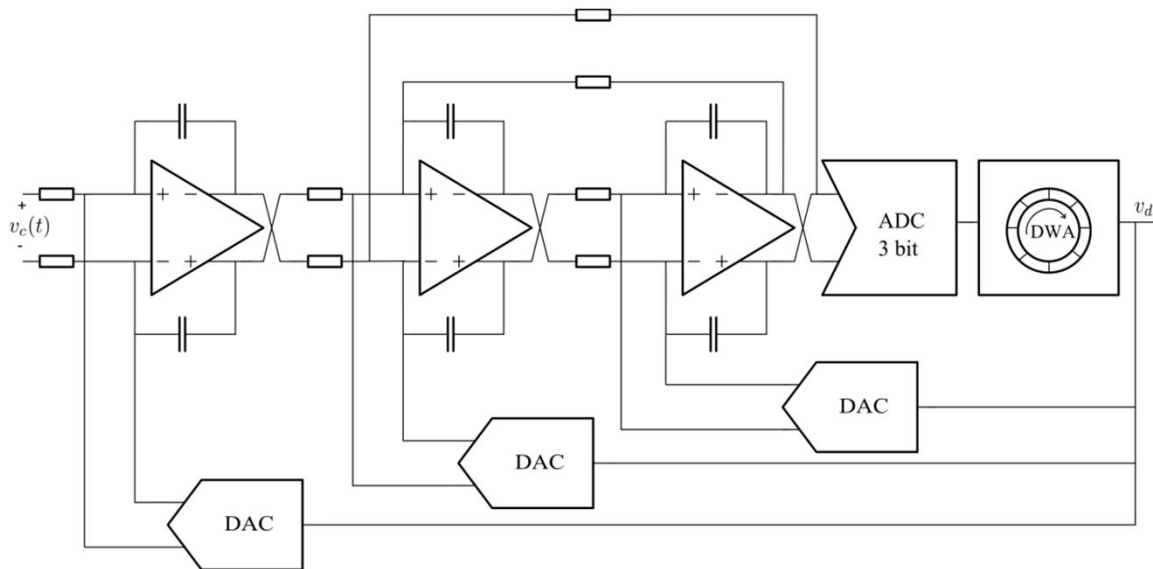
# Continuous-Time $\Delta\Sigma$ ADC for LTE (FP7 DRAGON project, SoS)

Mattias Andersson


- 3<sup>rd</sup> order, 3-bit,  $f_s=288\text{MHz}$ ,  $\text{BW}=9\text{MHz}$  ( $\text{OSR}=16$ )



**Tayloring the feedback pulses for the three DACs,  
the 4<sup>th</sup> DAC around the quantizer is avoided!**




# Design details

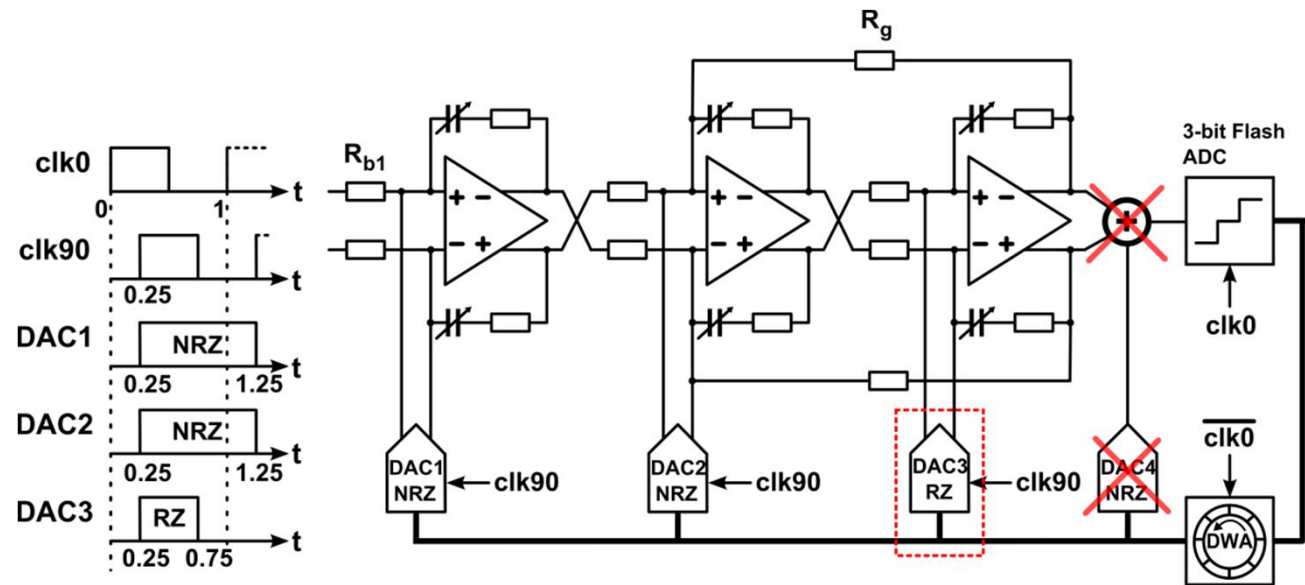


RZ pulses in DAC3 reduce sensitivity to loop delay  
Loop delay compensation (DAC4) can be omitted  
Quadrature clock phases assumed (available "for free" in any radio RX)




# Measurement results

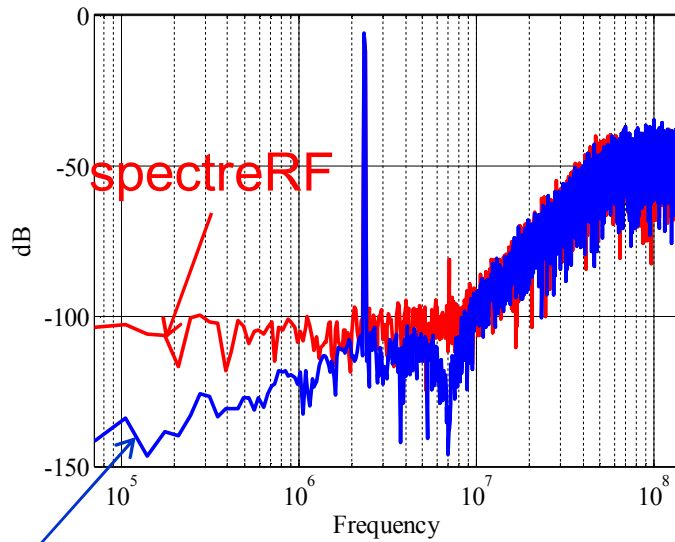

 Very good predictions  
with spectreRF +  
transient noise




**Peak SNDR 69dB**    **Peak SNR 71dB**

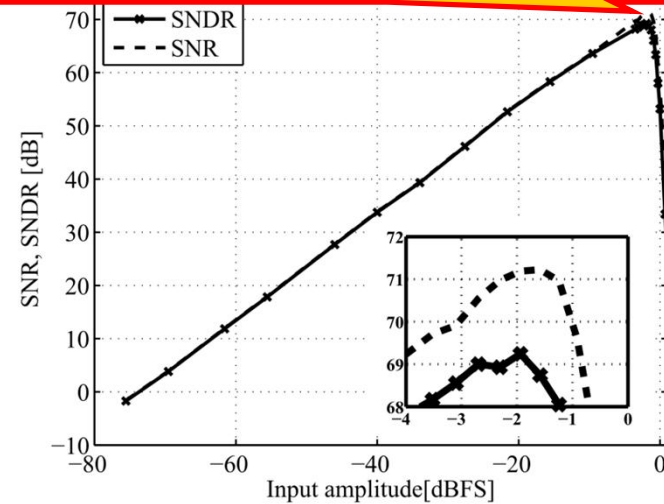

# Chip photograph and performance summary

To be presented at the A-SSCC 2012

## 65nm CMOS

 


Parameter	Value
<b>BW</b>	<b>9MHz</b>
<b>OSR</b>	<b>16</b>
<b>SNDR</b>	<b>69dB</b>
<b>I<sub>vdd</sub></b>	<b>6.2mA</b>
<b>FOM</b>	<b>175fJ/conv step</b>
<b>Area</b>	<b>0.1mm<sup>2</sup></b>

**Improved version with added filtering action:  
TO in June 2012 (not yet received), and again in Oct. 2012**

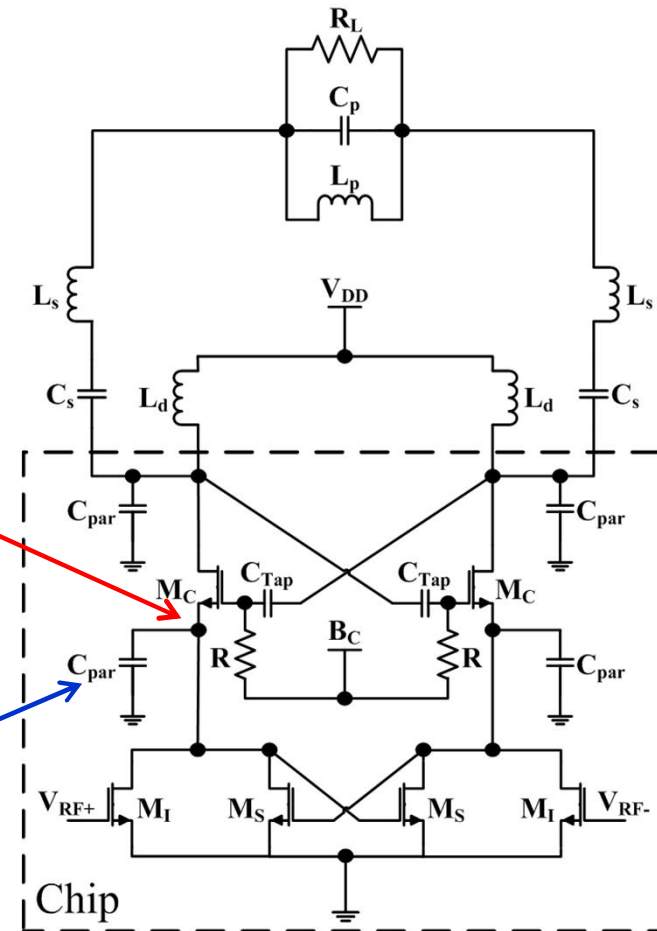
# Power Amplifier in 65nm CMOS (VINNOVA, SoS)

Jonas Lindstrand

- Self-oscillating PA
  - Supply ( $V_{dd}$ ) modulation
  - Reduced switching losses
- Wideband injection lock
  - Resistive injection node
  - $M_S$  amplifies injected current
- Tapped cascode
  - $C_{Tap} + C_{par,Mc}$
  - Reduced stress on  $M_I/M_S$
  - Reduced “SC” loss on  $C_{par}$




# Chip photograph and performance


 


Presented at ESSCIRC 2011

Output power

 


PAE

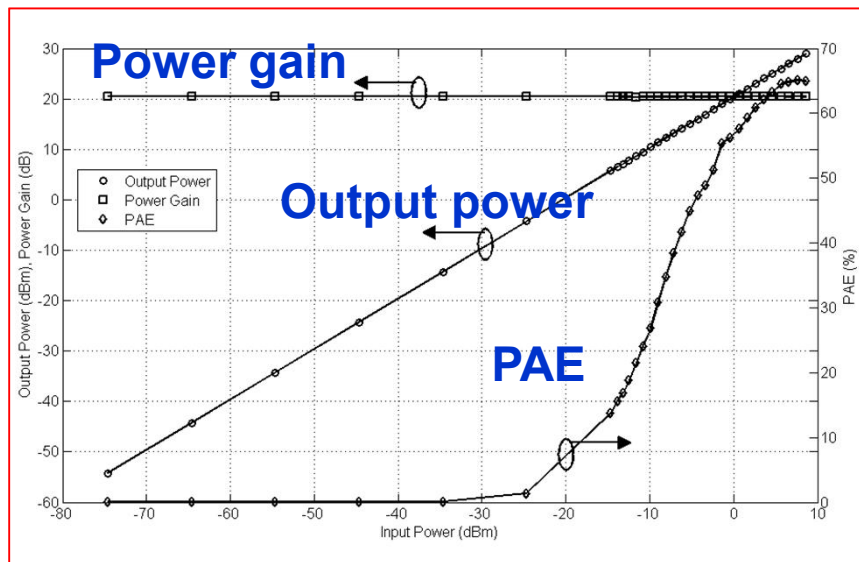 


# LO generation (VCO, active-PPF, 3/2 divider)

Reduces VCO pulling from PA

with M. Törmänen  
and A. Axholt




 


30mW Power Consumption

 




# LO generation – performance

   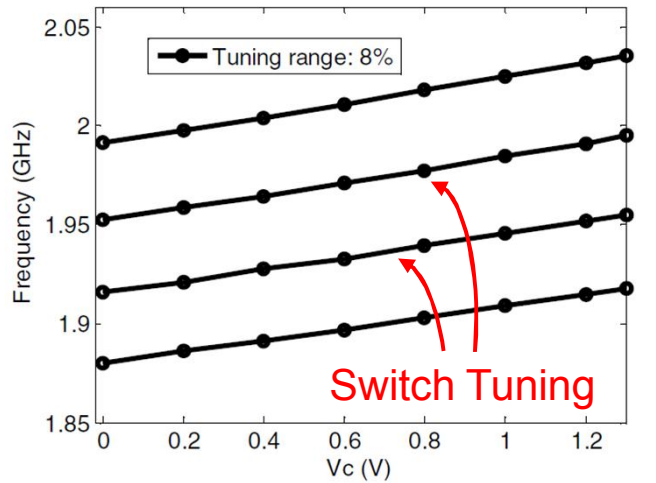
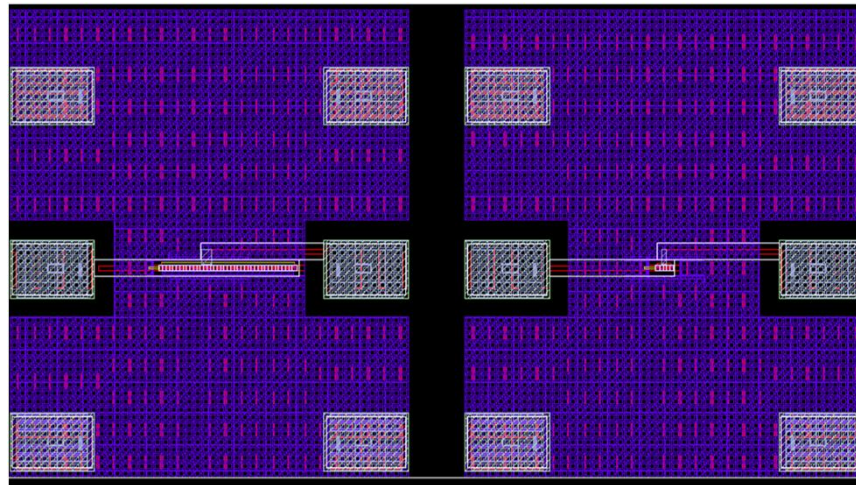
# Models for ED-MOS in STM 65nm CMOS

---


- Increase PA output power
  - Use ED-MOS transistors with high breakdown voltage
- No real RF model is supplied from CMP
- We will build our own RF MOS model
- Together with Prof. Christian Fager at Chalmers


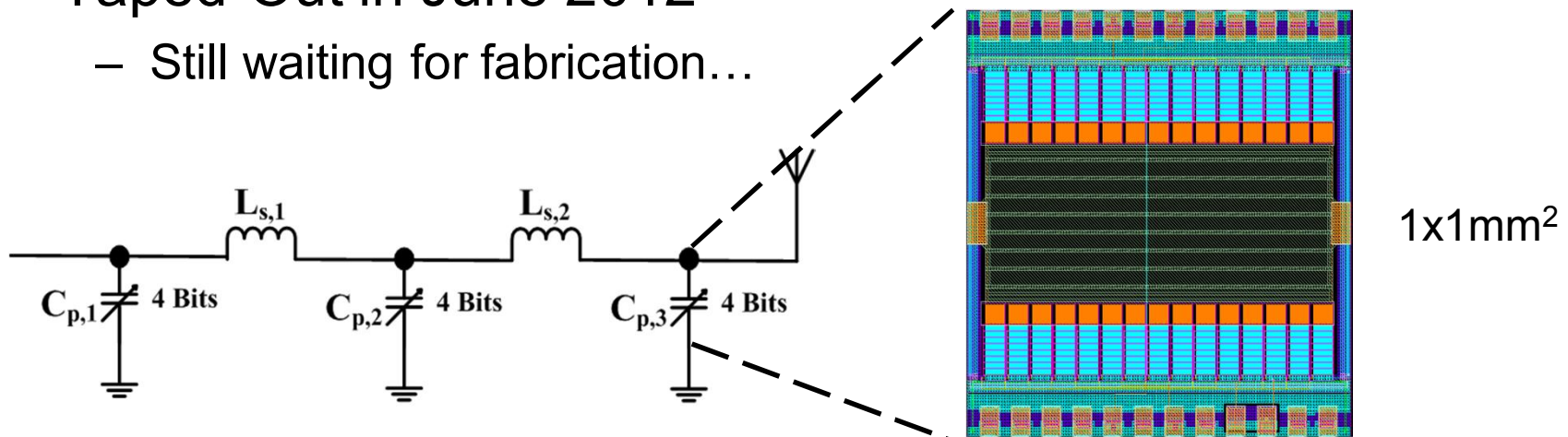
# 700-900MHz Impedance Tuner in STM 65nm CMOS-SOI




- Compensate for the antenna mismatch
  - Up to a VSWR of 4.5
- Low insertion loss (IL)
  - Less than 1dB with off-chip inductor Q of 50 for  $L_{s,1}$  and  $L_{s,2}$
- 4-bit switched capacitor banks ( $C_{p,1}$ ,  $C_{p,2}$ ,  $C_{p,3}$ )
  - Can handle 30dBm of TX power at an antenna VSWR of 4
- Taped-Out in June 2012
  - Still waiting for fabrication...


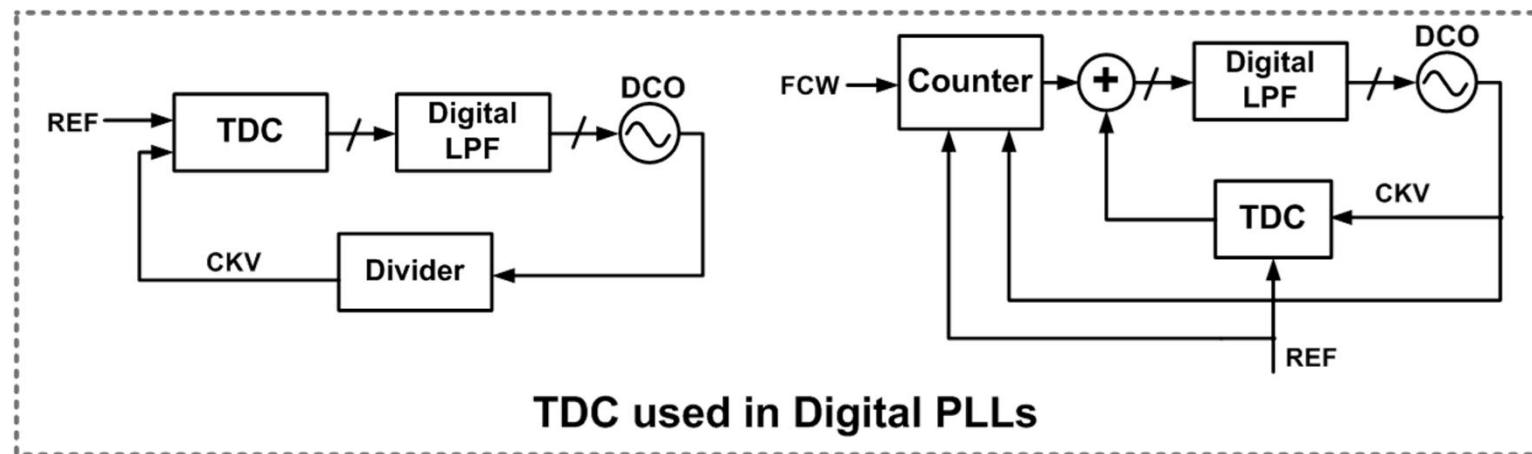
# Time-to-digital converter (VR, SSF DARE, EU Marie Curie)

Ping Lu

- TDC in digital PLL replaces phase-frequency detector of analog PLL




- Smaller TDC-cell delay ( $\Delta t_{\text{delay}}$ )  $\rightarrow$  lower in-band PLL noise



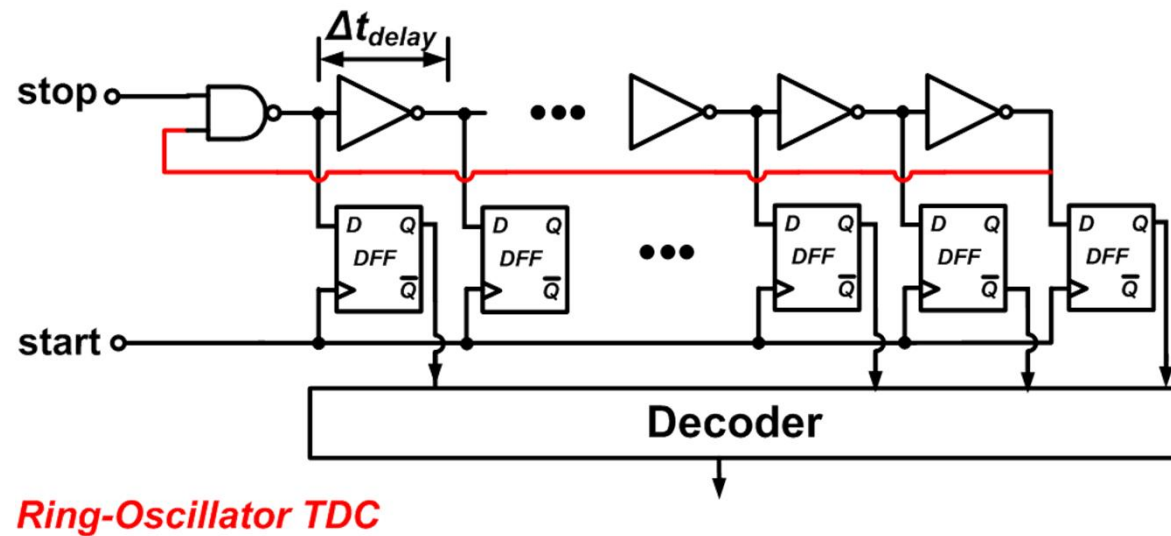
# Ring-oscillator TDC

- Ring-Oscillator TDC → large detection range with few stages



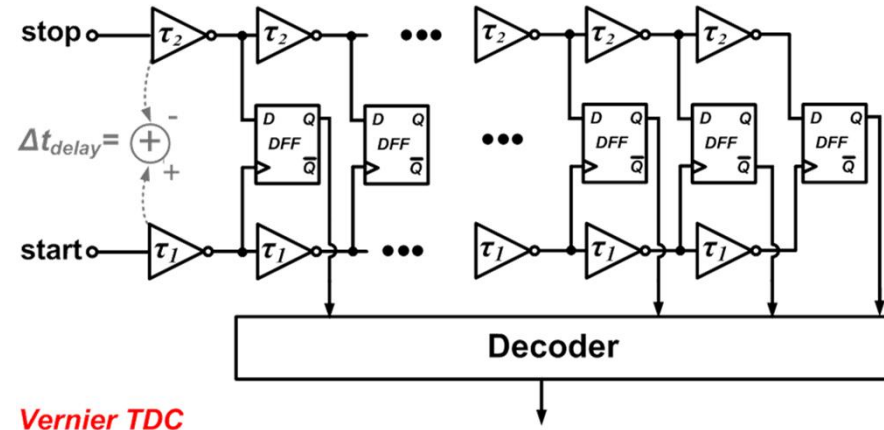
# Vernier TDC and GRO TDC

- Vernier TDC  $\rightarrow \tau_1 - \tau_2 = \Delta t_{\text{delay}} < \tau_1$  ( $\tau_2$ )
  - However, a very large number of stages are required




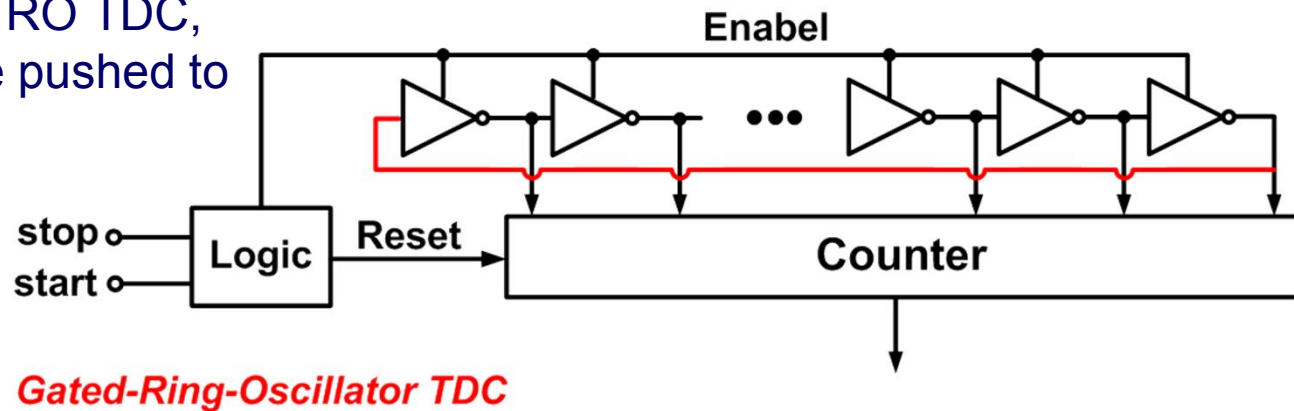- Ring-Oscillator (RO) TDC  $\rightarrow$  large detection range with few stages
- ✓ Gated-RO TDC  $\rightarrow$  as RO TDC, with quantization noise pushed to high frequencies



# Vernier + gated ring oscillator



- New TDC → combines Vernier + GRO

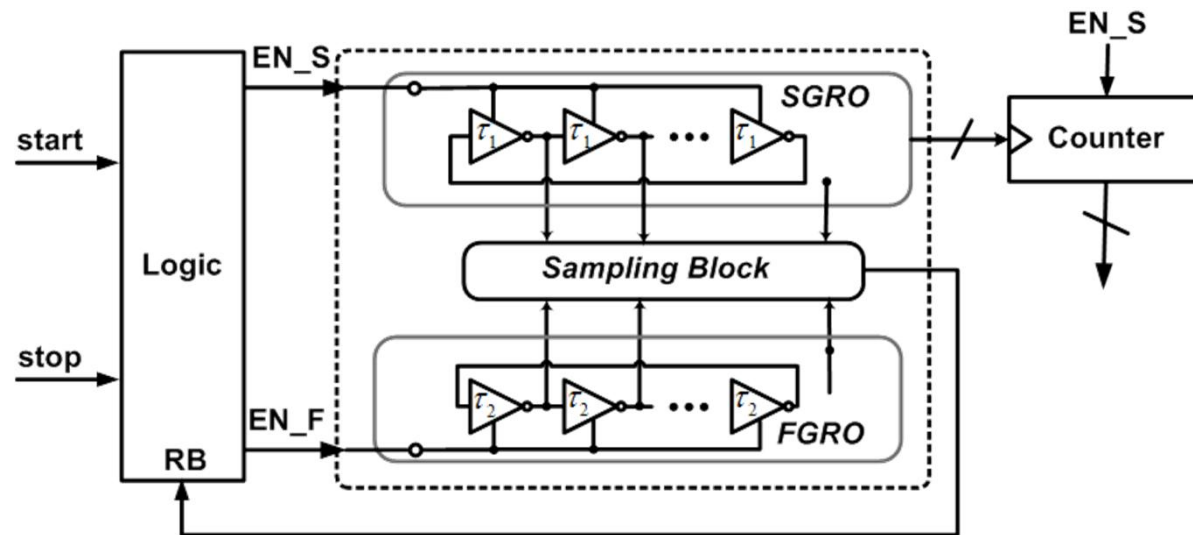

**High Vernier time resolution + First-order noise shaping**


  
# Chip photograph and results of VGRO TDC



<b>Area</b>	<b>0.027mm<sup>2</sup></b>
<b>Process</b>	<b>90nm CMOS</b>
<b>Current (Supply)</b>	<b>3mA (1.2V)</b>
<b>Vernier resolution</b>	<b>~5ps</b>
<b>Effective in-band resolution (OSR= 16)</b>	<b>~3ps</b>


**Presented at ESSCIRC 2011**

**Invited and  
published in JSSC  
July 2012**





# Two-dimensional VGRO TDC

 


- Developed from VGRO TDC and 2-D Vernier (Univ. of Pavia, Italy)
- Many more signal pairs used than in 1-D VGRO TDC → enhanced detection range
- Reduce latency time
- Under measurement, to be presented at NORCHIP 2012



Vercesi et al, JSSC Aug. 2012




# Chip photo and simulations

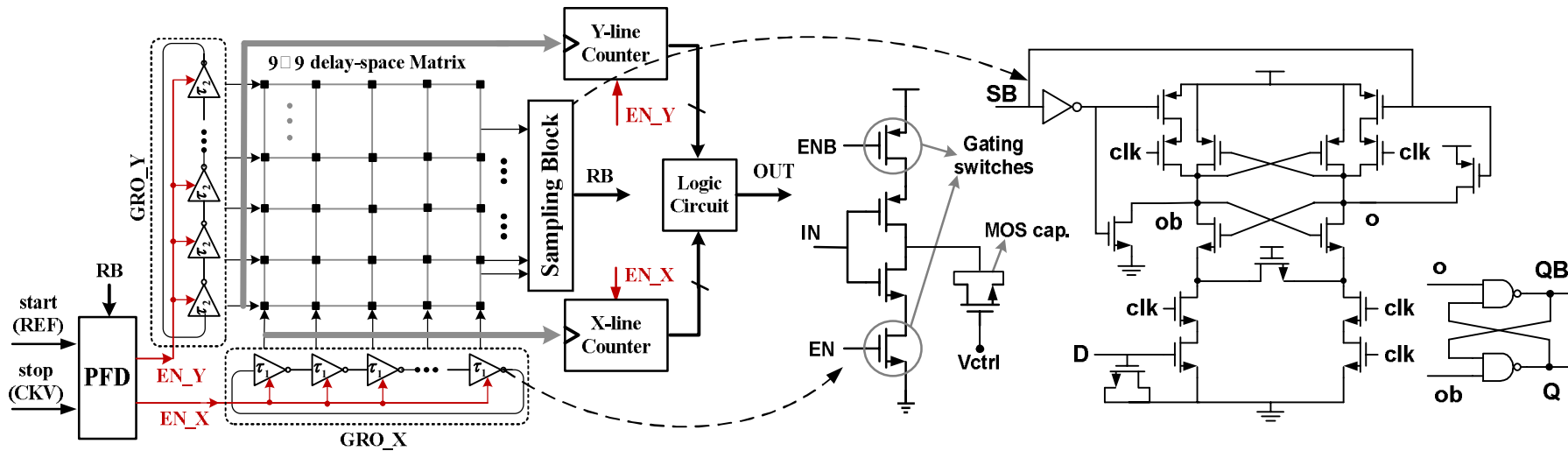

GRO based 2-D Vernier TDC implementation

  

Transient output

 

PSD of TDC output





**SCANDINAVIAN EXCELLENCE  
DEFINED IN LUND**



**LUND**  
UNIVERSITY

