

E-band SiGe Beamsteering Transmitter Building Blocks

2014-09-12

Tobias Tired

Electrical and Information Technology Lund University



Presentation outline


- **E-band wireless backhaul**
- **Beam forming concept**
 - Linear timed and phased arrays
- **Transmitter architecture**
- **Designed building blocks**
 - 28 GHz QVCO with I/Q phase error tuning and detector
 - 28 GHz to 1.75 GHz Divider
 - PA version 1
 - PA version 2
 - PA version 3: diploma thesis
- **Conclusions**



E-band wireless backhaul


- The E-band at 71-76 GHz and 81-86 GHz: wireless point-to-point communication

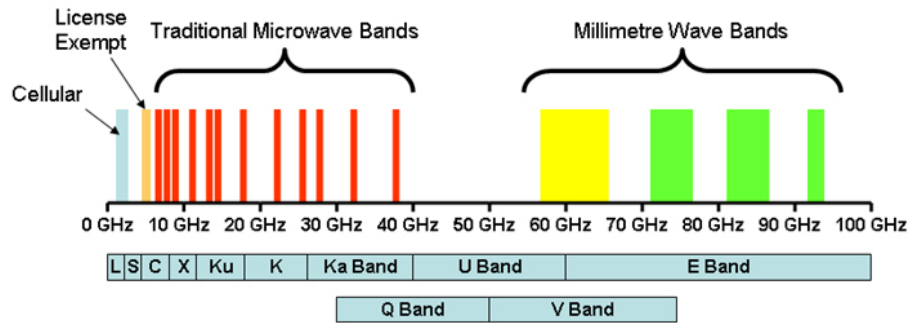- 5 GHz of spectrum \Rightarrow data rates of Gb/s



- costly optical fiber backhaul \Rightarrow wireless data link

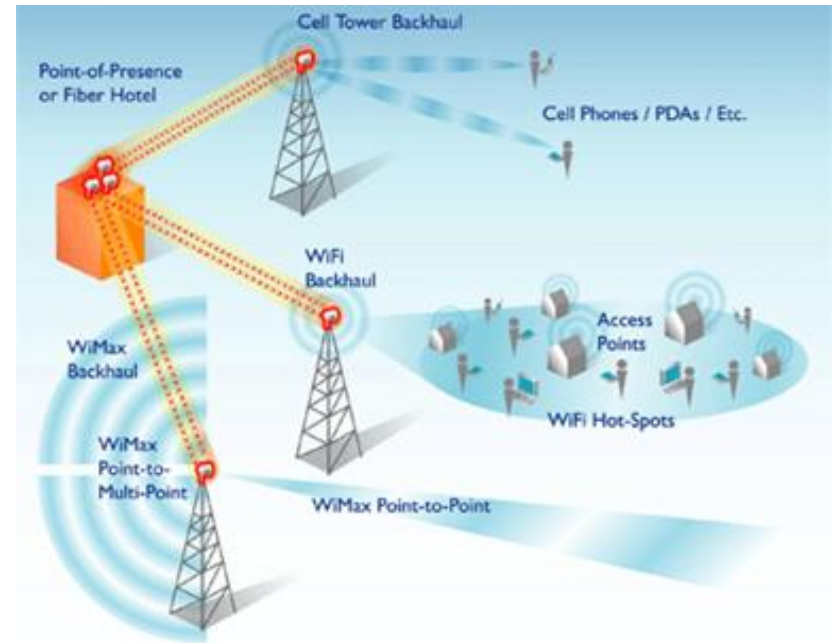- Heterogeneous networks: macro, pico and femto cells \Rightarrow **large number of base stations**




A wireless backhaul is highly advantageous



Beamsteering concept

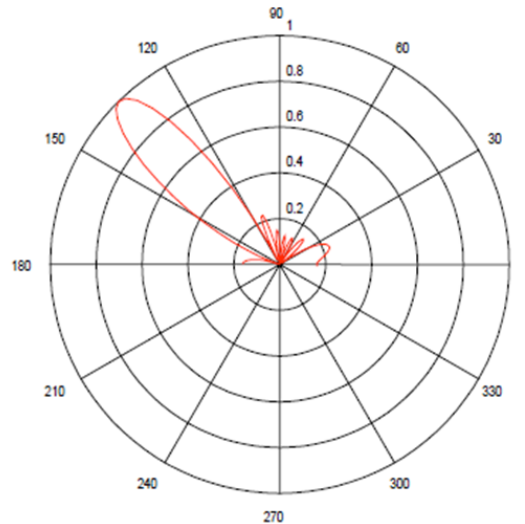- Beamsteering \Rightarrow equal to spatial filtering of radio signals
- Array of antennas \Rightarrow steered to block transmission to certain directions and to provide antenna gain to a desired direction




- Applications:

- Radio communication
- Surveillance
- Radar
- Sonar
- Audio



Linear timed arrays

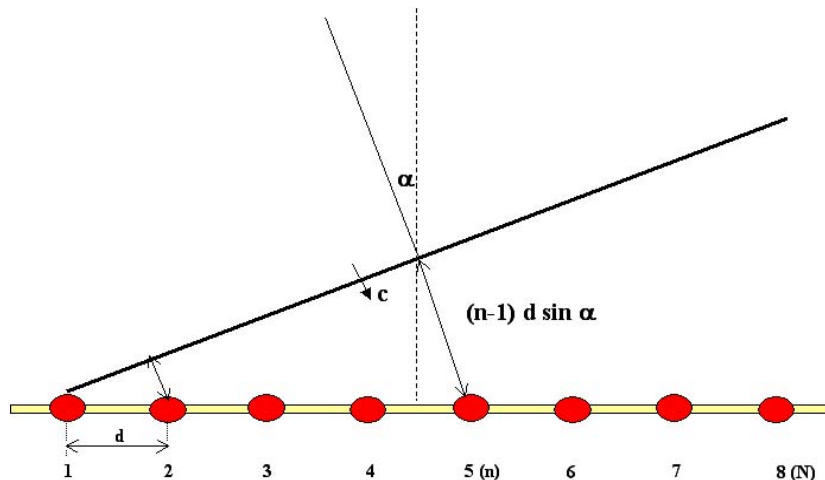- Linear equally spaced array with 8 TX antenna elements
- Wave plane at transmit angle α



- Different time of departure Δt

$$\Delta t = \frac{(n-1)d \sin \alpha}{c}$$

c = light speed, d = element spacing

- Beamforming transmitter: aligns the signals to the antenna elements in time

⇒ **Coherent combination to one direction and suppression to other directions**

Use a small fractional BW ⇒ Realization of time delay with **fixed phase shift** ⇒ **Linear phased array**



E-band transmitter architecture

Unpublished material



28 GHz QVCO plus phase error detector and tuner

Unpublished material



QVCO phase error detector

Unpublished material



28 GHz QVCO with phase error detector and tuner

Unpublished material




Divide by 16

Unpublished material




Beam steering implementation with PLL

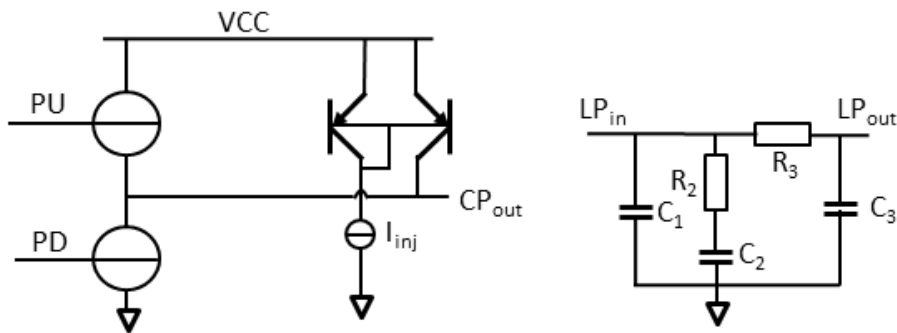

Unpublished material




Power amplifier architecture

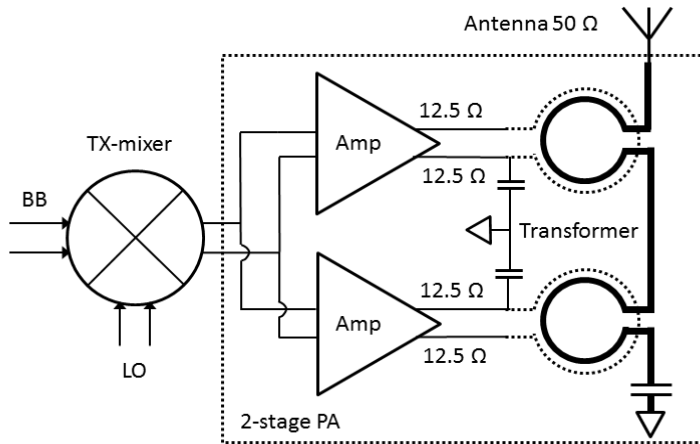


50 Ω antenna impedance transformed to 12.5 Ω \Rightarrow lower VCC

Stage 1 and 2
Version 1

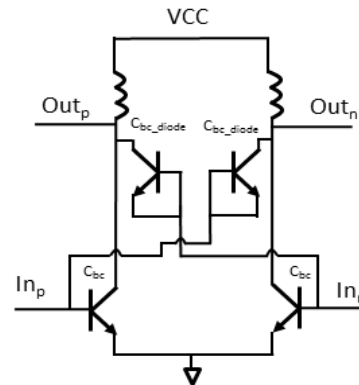


Stage 1
Version 2

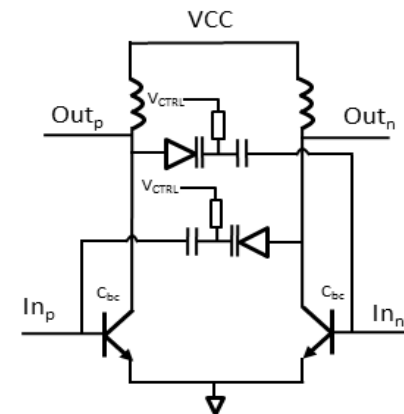


Capacitive cross coupling with diode connected devices to neutralize base collector capacitance




Power amplifier transformers

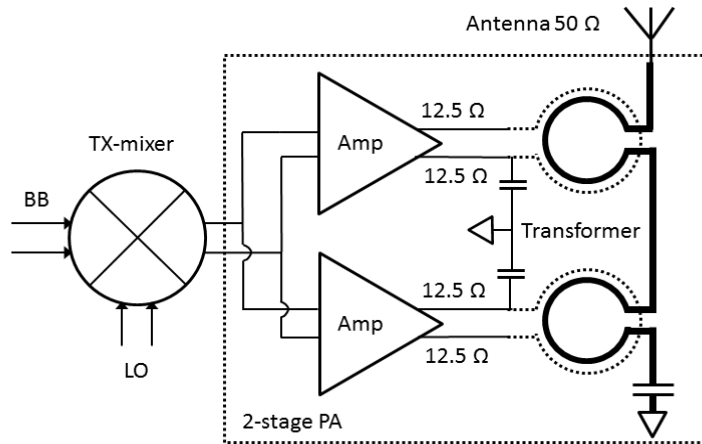

Input transformer

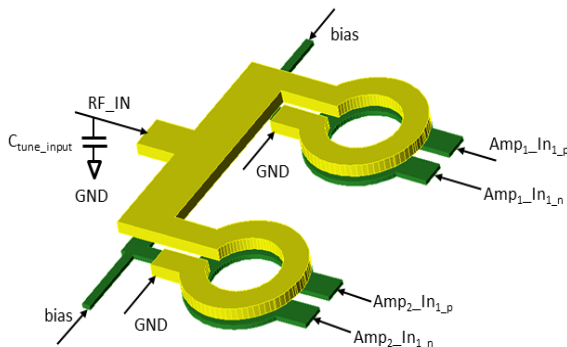




Output transformer

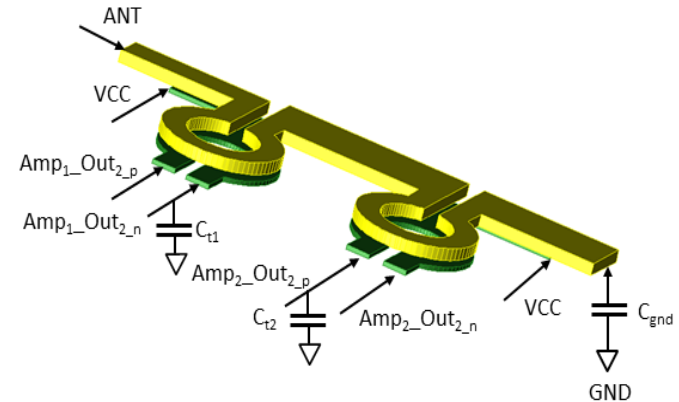

- **50 Ω antenna impedance transformed to 12.5 Ω single ended \Rightarrow lower VCC for same CP_{1dB}**
- **Tuning capacitors: reduce imbalance for improved power combination**
- **Input transformer: 50 Ω antenna impedance to 100 Ω differential for each amplifier**



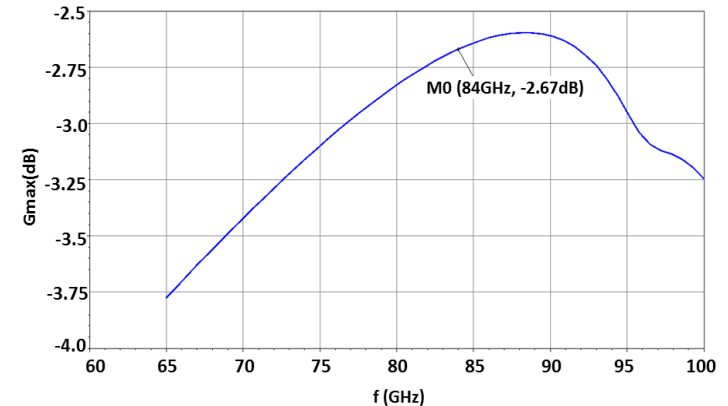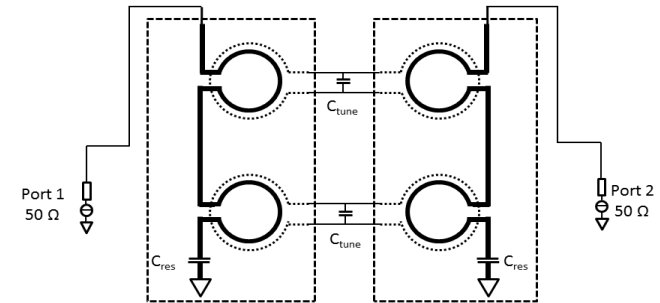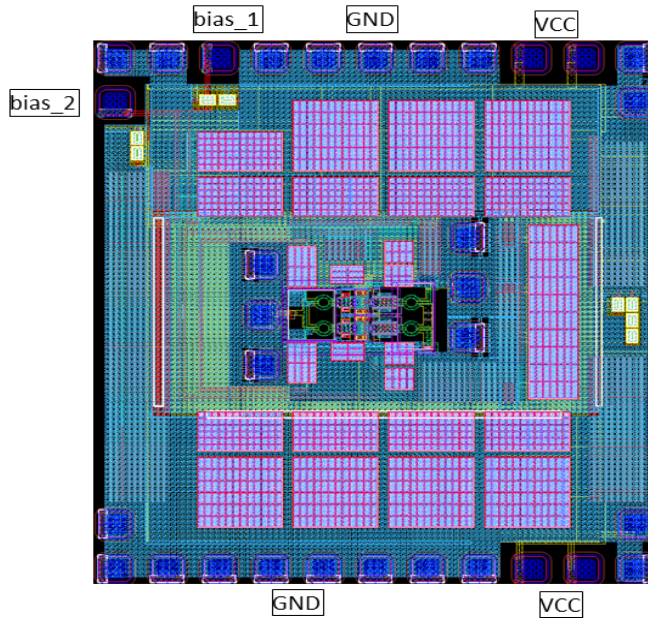Transformer simulation results and chip layout



- Chip area: 0.87 mm²
- Output transformer loss: two transformers back to back $\Rightarrow G_{max} = -2.67$ dB
 $\Rightarrow 1.34$ dB loss for one transformer



Power amplifier simulation results

Version 1

Unpublished material



Power amplifier simulation results



Version 2 – gain versus varactor voltage

Unpublished material



Power amplifier diploma thesis

Version 3 by Manuel Beljano

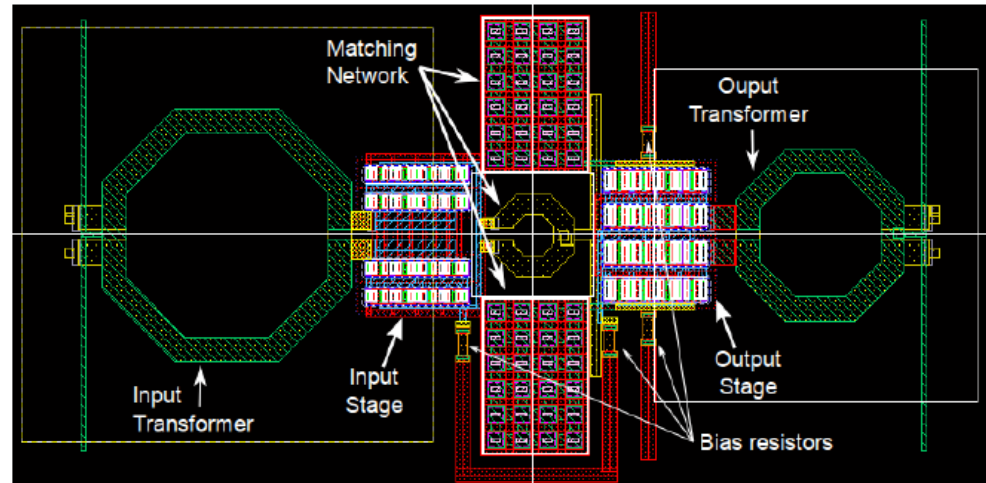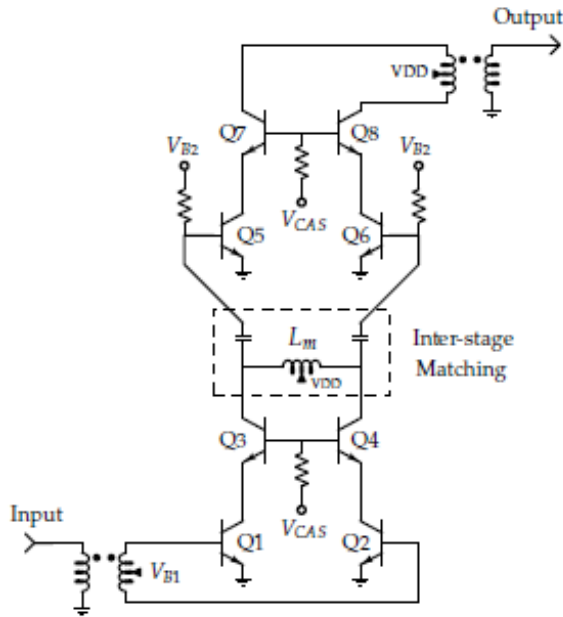


- Cascode architecture
- $V_{CC} = 3.5 \text{ V}$





Power amplifier simulation results

Version 3: diploma thesis

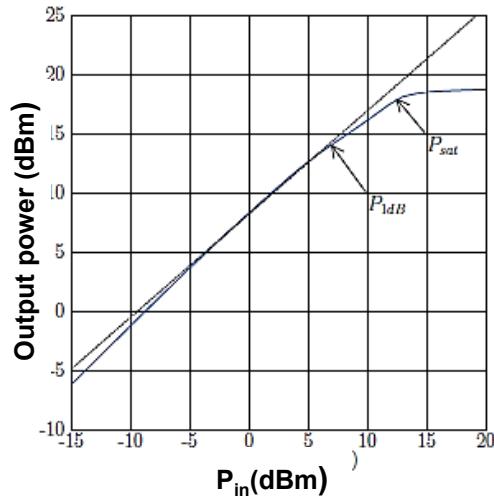

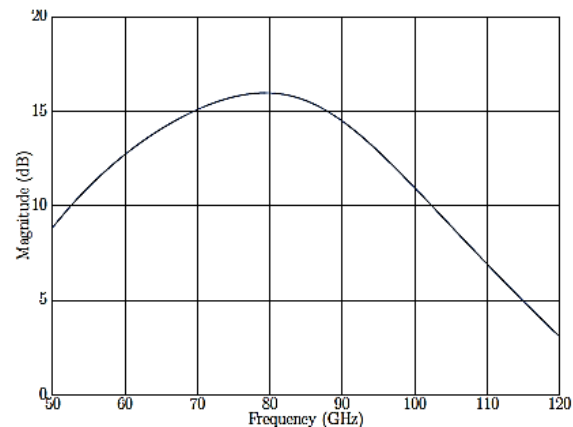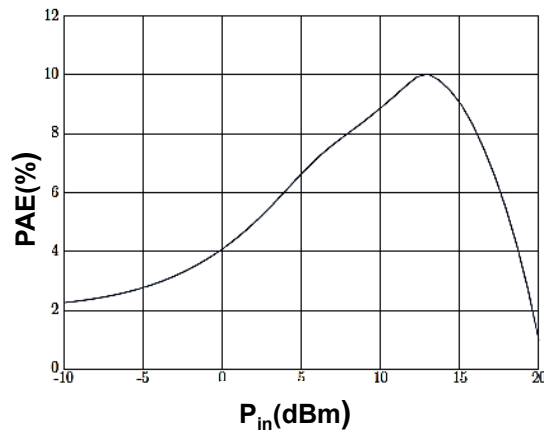VCC = 3.5V
Gain = 16 dB
PAE = 7.5 % at CP_{1dB}
CP_{1dB} = 14.1 dBm
P_{sat} = 18 dBm



Conclusions

- **Project status September 2014**
- **Designed TX blocks: 28 GHz QVCO**
 - Three power amplifiers
 - Divider
 - PLL with phase control
- **Remaining TX blocks: 28 GHz I/Q mixer**
 - 84 GHz mixer
- **Complete beam steering transmitter to be taped out in December 2014**

