



CMOS Switched-R-C Techniques for Interference Rejection and Self- Interference Cancellation

Eric Klumperink


A. Ghaffari, D.J. v.d. Broek, B. Nauta

University of Twente, CTIT, IC Design


Enschede, The Netherlands

Trend to remove dedicated filtering

❑ Armstrong 1915

 

❑ Dream

 


Key Observations:


- ❑ Trend Analog \Rightarrow Digital
- ❑ Still analog needed for feasibility
- ❑ Flexibility \Leftrightarrow less RF pre-filtering
- ❑ Different names:
 - “SAW-less”
 - “Inductorless”, “wideband”
 - Reconfigurable
 - Software Defined Radio (SDR)
 - Cognitive Radio
- ❑ Focus on flexible techniques to:
 - Handle blockers \Leftrightarrow high CP1dB, IIP3 needed
 - Reject interference flexibly \Leftrightarrow filter/cancel selectively

Compression Problem

 - ❑ $P_{RF} = 0 \text{ dBm} \Leftrightarrow 1 \text{ mWatt} \Leftrightarrow .63 \text{ V}_{\text{pk-pk}}$ in 50Ω
 - Typical supply: $V_{DD} = 1.2 \text{ V}$
 - 6dB gain \Leftrightarrow clip to V_{DD} !




 - ❑ Compression:
 - reduced gain: $A_2 < A_1$
 - ...to hard clipping/blocking
 - renders "Cross-modulation"
 - Higher order distortion terms (IIP3/IIP2 model NOT valid!)
 - Higher Noise Figure ("Blocker NF")




How to cancel strong blockers?

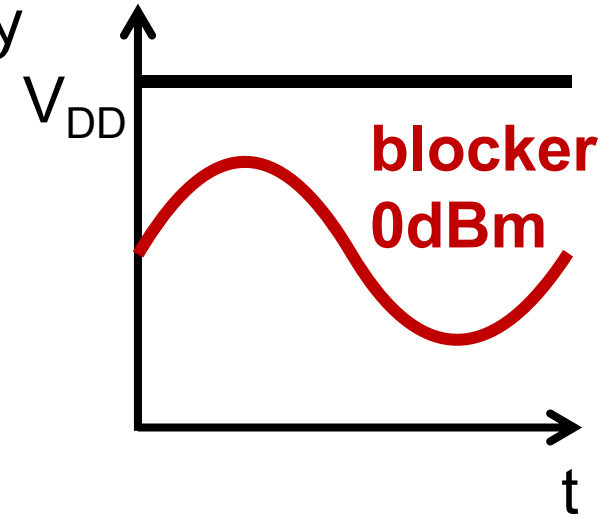- ❑ Gain \Leftrightarrow clipping and nonlinearity
- ❑ Start Passive, reject “upfront”!!
- ❑ Traditionally:
 - SAW-filter: fixed frequency
 - L-C “tracking” filter: $\omega_0 = \frac{1}{\sqrt{LC}}$ (limited tuning-range, limited Q and big size)
- ❑ More flexibility: clocked switches + R + C
 - Interference cancelling high CP1dB Notch filter
 - Self-Interference Cancelling Full-Duplex Rx




Notch Filter via Switched-Cap Network

□ RLC model:

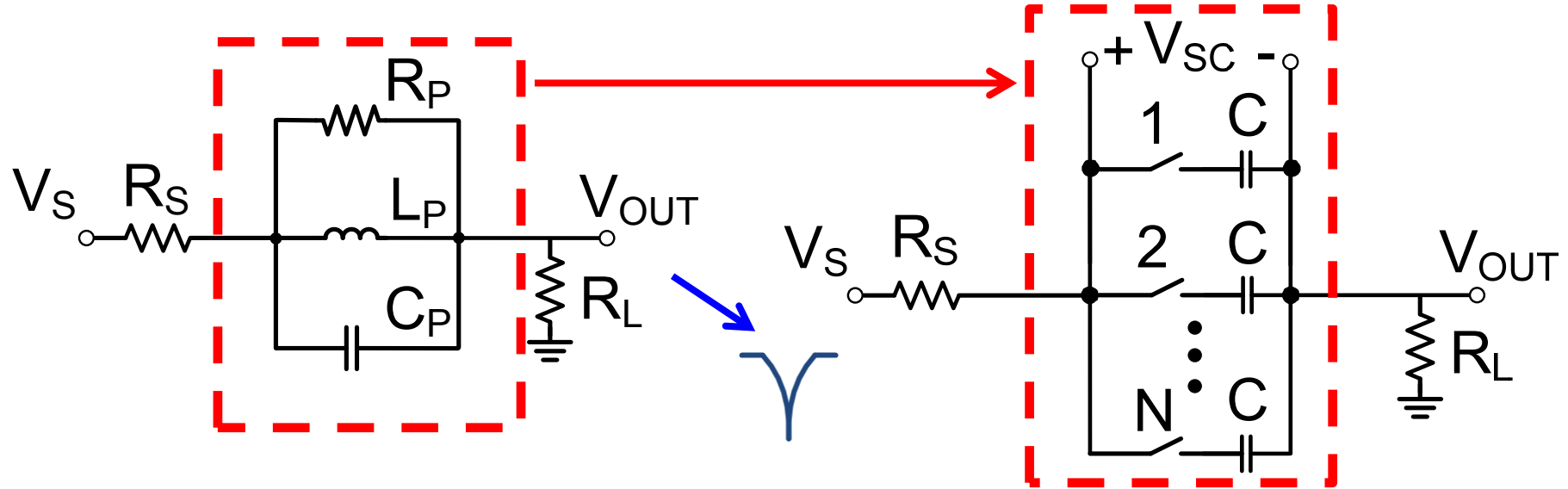


□ R_p is preferably high

 □ Clock frequency
 \Leftrightarrow notch frequency




N-Path Notch Filter

$RC \gg T_s/4$


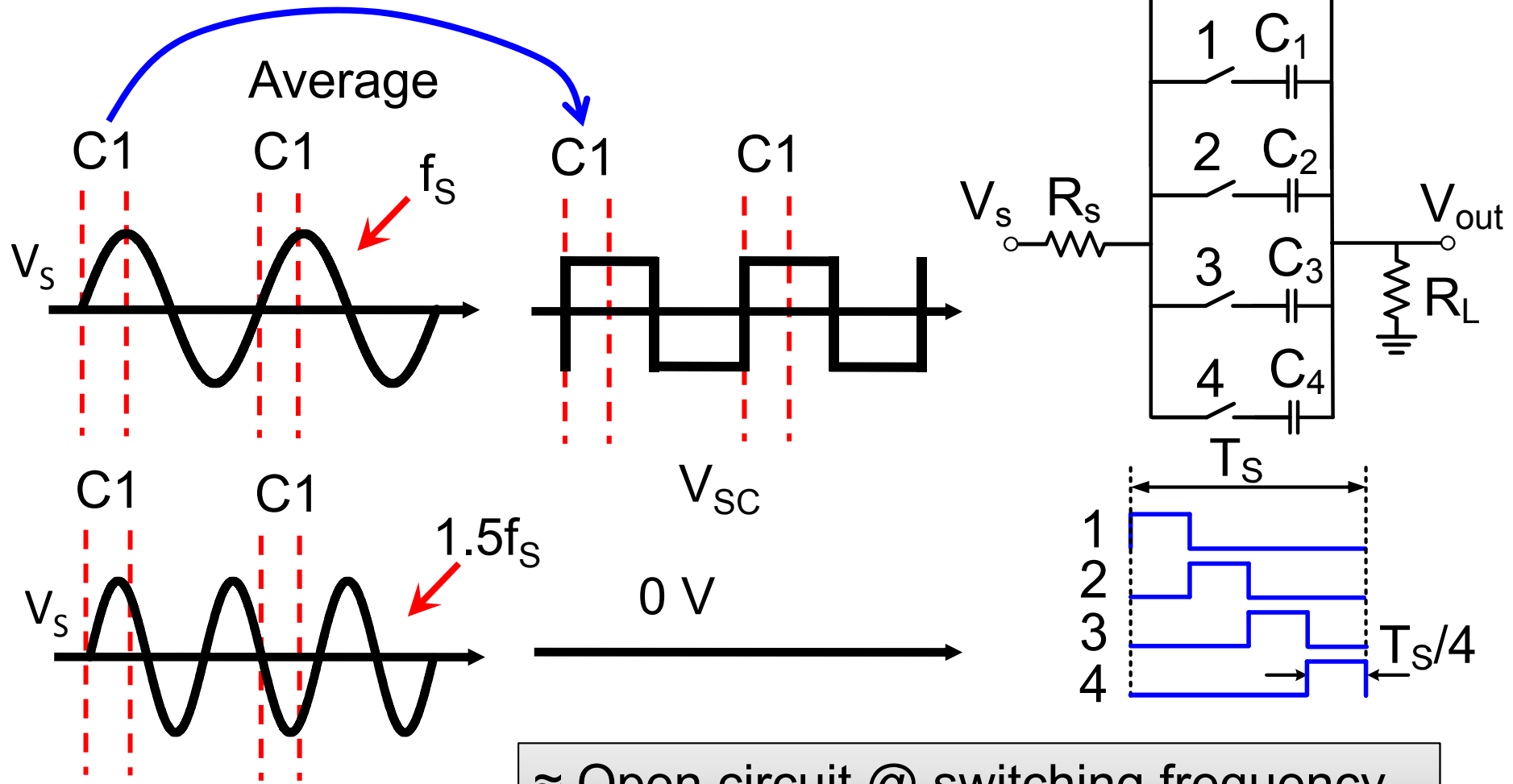


\approx Open circuit @ switching frequency
 \approx Short circuit @ other frequencies

Notch= Up-Converted High-Pass Filter

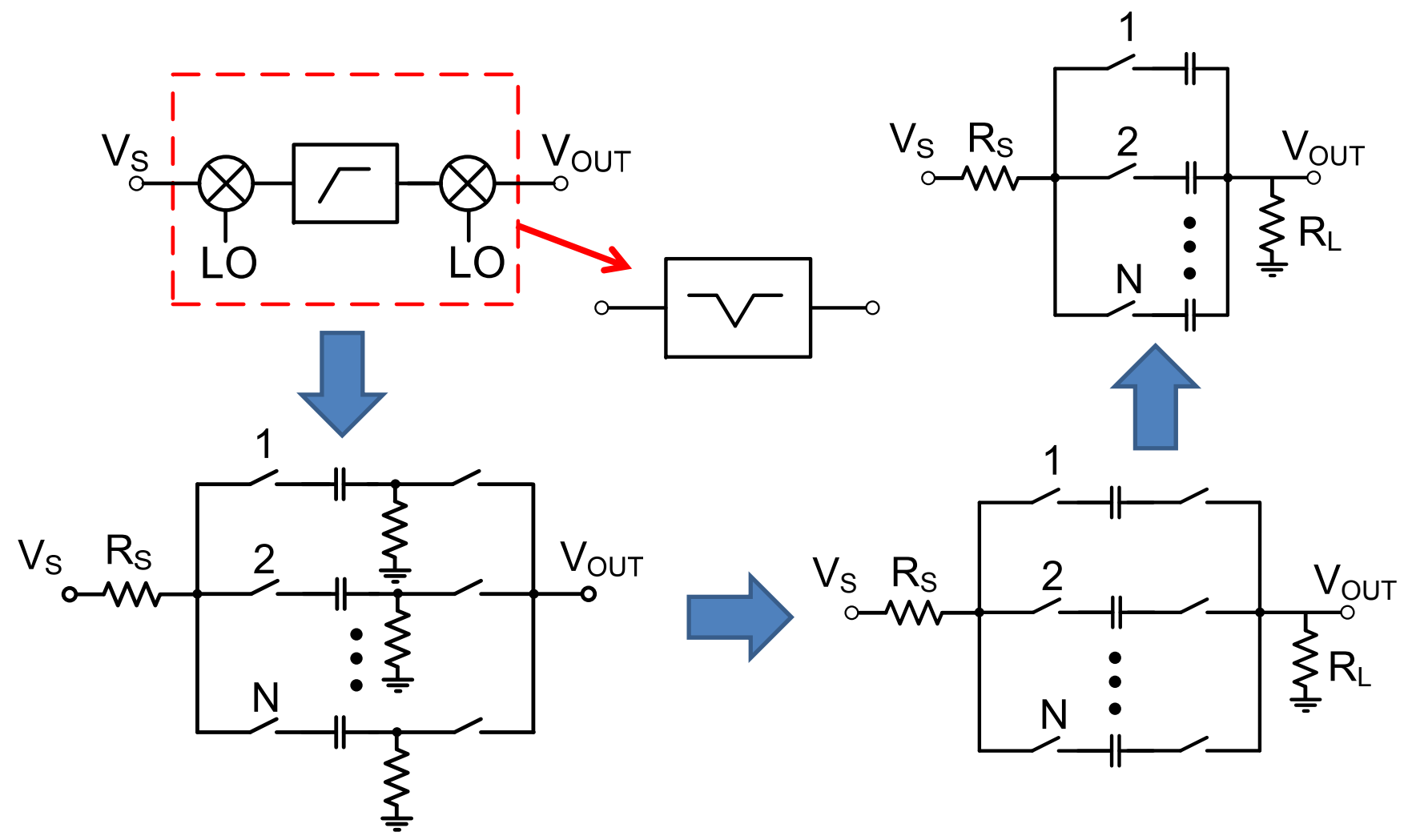

8-path Notch-Filter

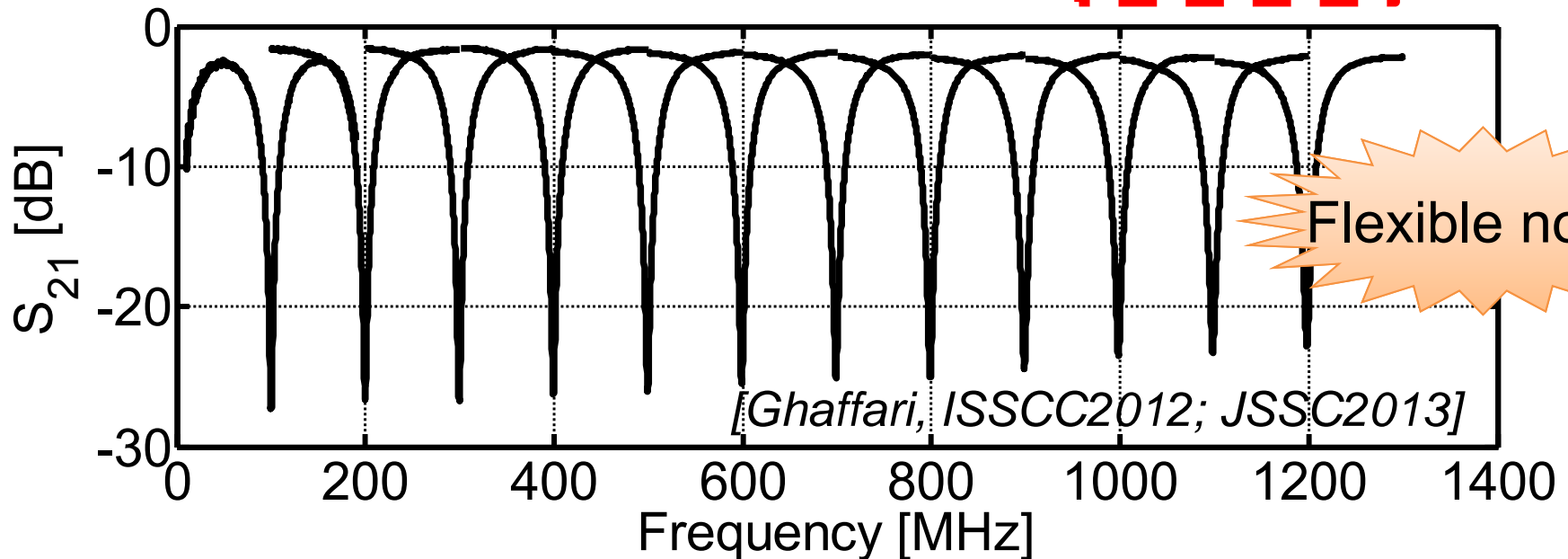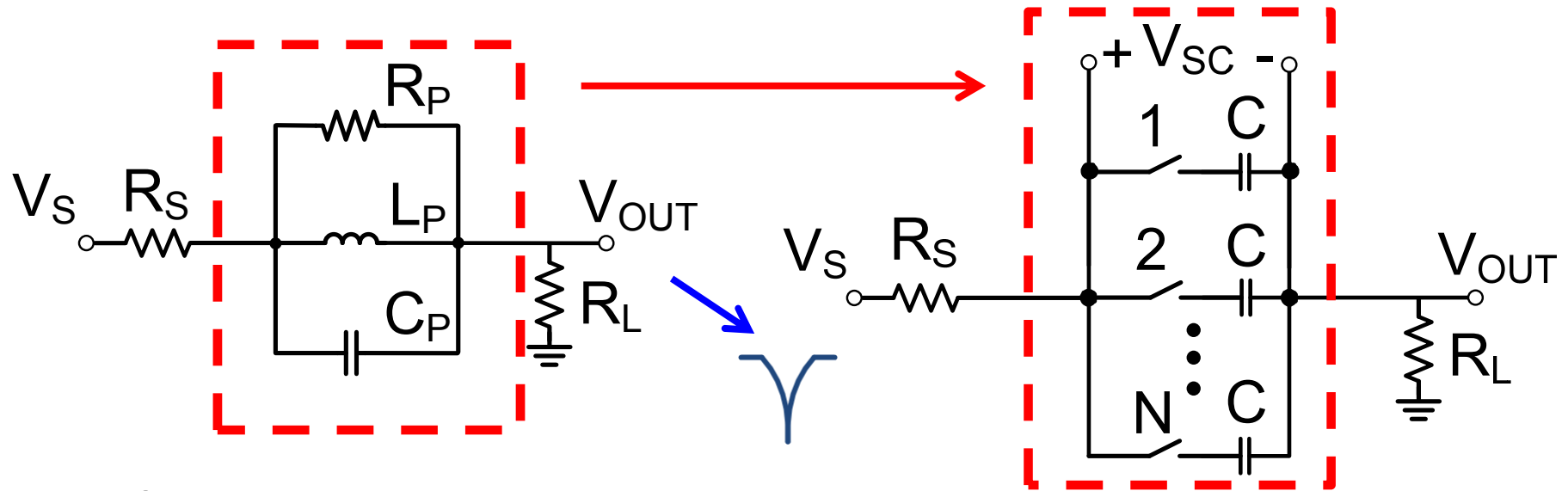


[Ghaffari, ISSCC2012; JSSC2013]

Approximate RLC Model

$$R_P = \frac{N^2 (1 - \cos(2\pi / N))}{2\pi^2 - N^2 (1 - \cos(2\pi / N))} (R_S + R_L)$$

$$C_P = \frac{N(R_P + R_S + R_L)}{2R_P} C$$

$$L_P = \frac{1}{(2\pi f_S)^2 C_P}$$

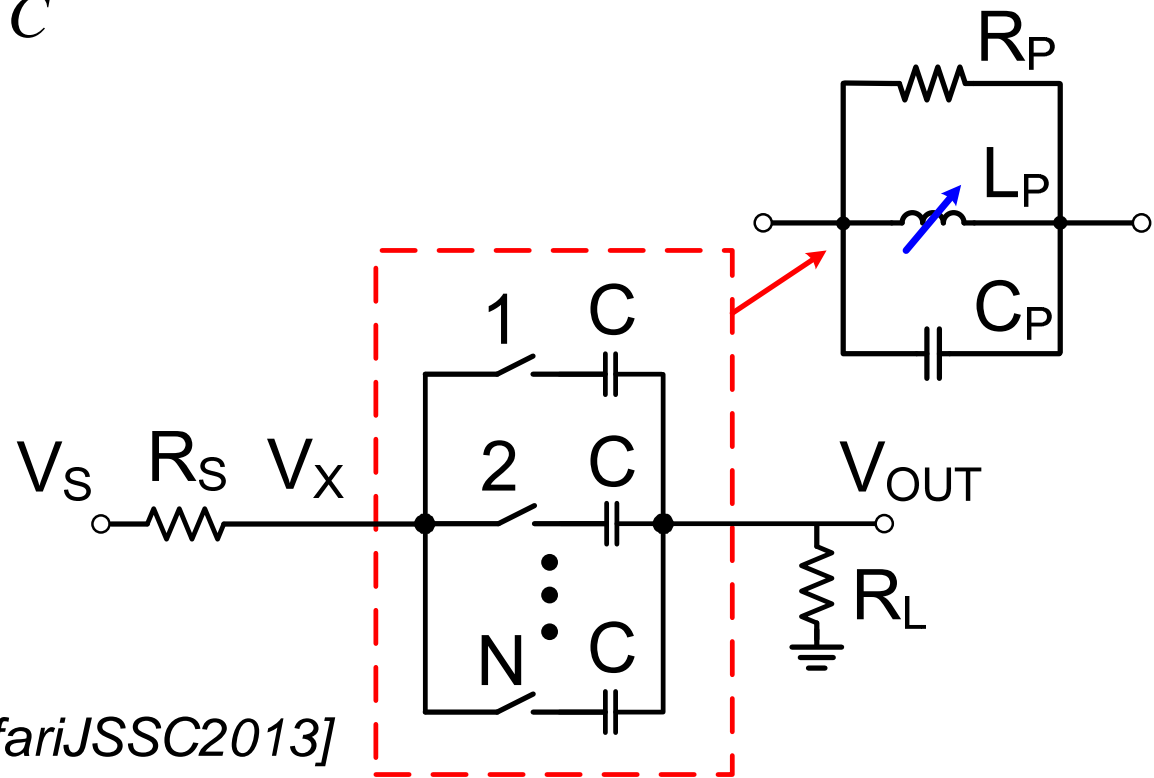

[GhaffariJSSC2013]

Benchmark

- ❑ [1] A. Bevilacqua et al., “A 0.13 um CMOS LNA with Integrated Balun and Notch Filter for 3-to-5 GHz UWB Receivers,” IEEE ISSCC Dig. Tech. Papers, pp. 420–421, Feb. 2007
- ❑ [2] J. Y. Lin, H. K. Chiou, “ Power –Constrained Third-Order Active Notch Filter Applied in IR-LNA for UWB Standards,” IEEE Trans. Circuits Syst. II, vol. 58, no. 1, pp. 11-15, Jan. 2011.

Q-enhanced LC resonator embedded in an LNA

Comparison (I)

	Differential	Single-Ended	[1]	[2]
Technology	CMOS 65nm	CMOS 65nm	CMOS 0.13um	CMOS 0.18um
Active Area	0.87mm ²	0.87mm ²	1.6mm ² (*)	0.51mm ² (*)
Power	3.5mW-30mW	2mW-16mW	7.5mW	1.8mW
Max. Rejection	21dB	22dB	44dB	35.7dB
Rejection	>18dB over 6MHz	>18dB @ over 6MHz	>10dB over 20MHz	NA

(*) Notch Filter + LNA 5dB with -10dBm Blocker

Comparison (II)


	This Work Differential	This Work Sngl-ended	[1]	[2]
Gain	-1.4 to -2.8dB	-1.4 to -2.5dB	19.4dB(*)	14.7dB(*)
NF(dB)	1.6-2.5dB	1.2-2.8dB	3.5dB(*)	5.3dB(*)
P _{1dB} (dBm)	6	2-6	-9.4(*)	NA
IIP3(dBm)	> +17	> +18	-2.9(*)	-2.5(*)
LO Leakage (dBm)	< -60	<-75	-	-
Tuning Range	0.1-1.2GHz	0.1-1.2GHz	4.7- 5.4GHz	5.4-6GHz

(*) Notch Filter + LNA

**ISSCC '15 / JSSC Dec'15:
A Self-Interference Cancelling Receiver
for In-Band Full-Duplex Wireless
with Low Distortion
under Cancellation of Strong TX Leakage**

Dirk-Jan van den Broek, Eric Klumperink, Bram Nauta

 IC-Design group, University of Twente, the Netherlands



UNIVERSITY OF TWENTE.

In-band full-duplex wireless


- TX and RX *simultaneously* at *same* frequency
- Why?
 - Up to 2x spectral efficiency

In-band full-duplex wireless

- TX and RX *simultaneously* at *same* frequency
- Why?
 - Up to 2x spectral efficiency
 - Simplified / flexible frequency planning

In-band full-duplex wireless

 - TX and RX *simultaneously* at *same* frequency
- Why?
 - Up to 2x spectral efficiency
 - Simplified / flexible frequency planning
 - Reduced air interface delay (e.g. FD relaying)




In-band full-duplex wireless


- TX and RX *simultaneously* at *same* frequency
- Why?
 - Up to 2x spectral efficiency
 - Simplified / flexible frequency planning
 - Reduced air interface delay
 - Benefits / applications in higher layers
 - Simultaneous data & control
 - Reciprocal channel
 - ...?

In-band full-duplex wireless


- Why not? (1)

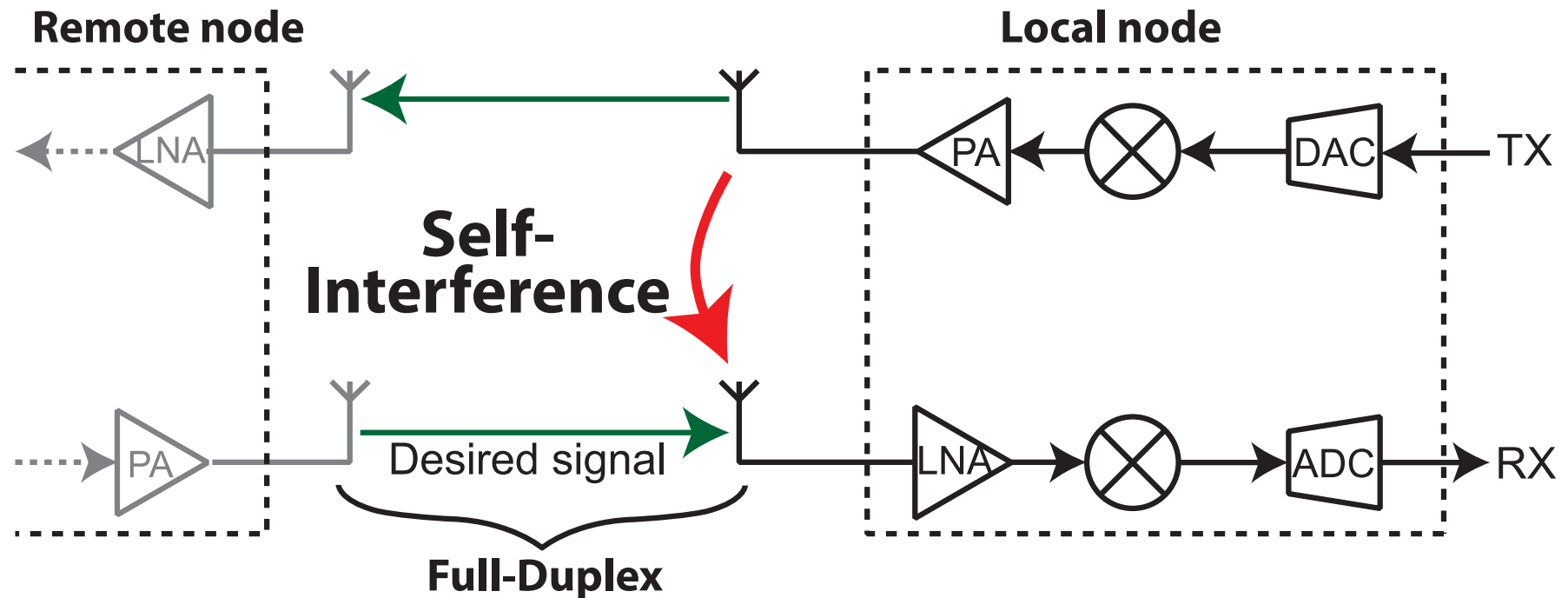

Challenge: Self-interference (SI)

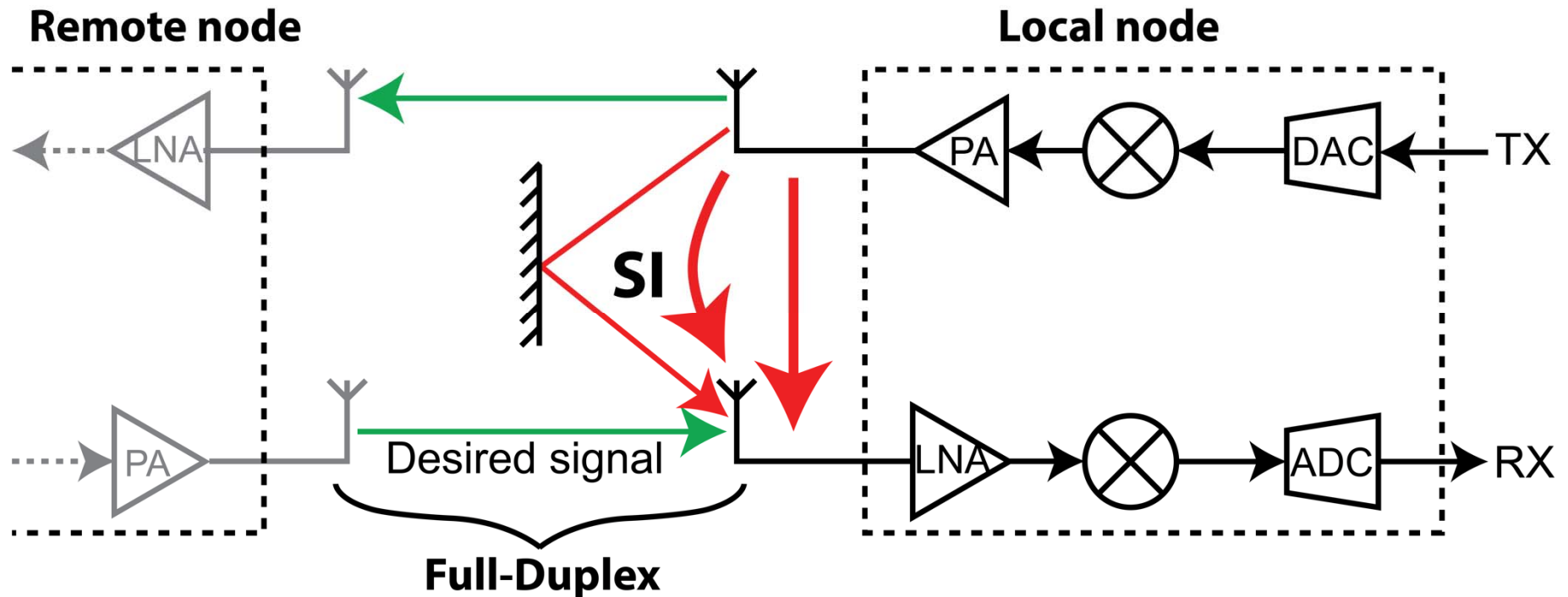

Challenge: Self-interference (SI)

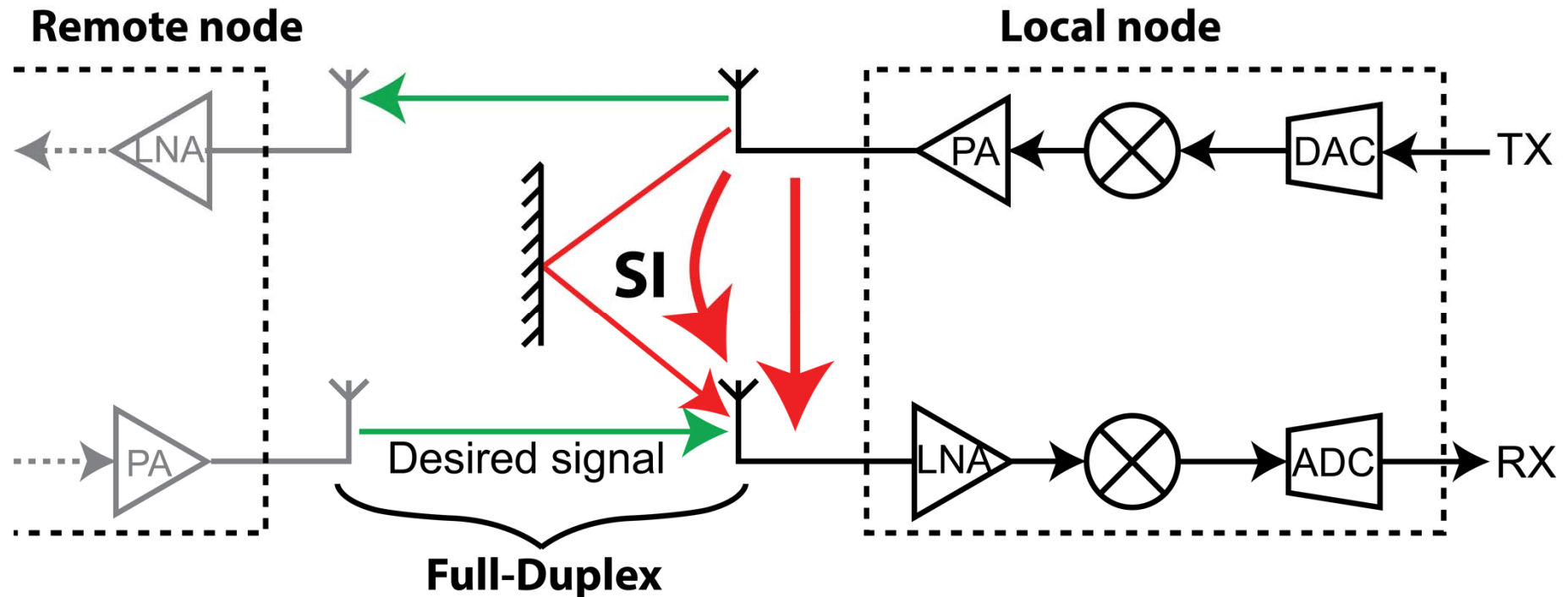


Short-range, relaxed low-power link:

16 MHz BW [WLAN], 10 dB NF \rightarrow -90 dBm noise floor

0 dBm TX power: \sim 90 dB total SI rejection desired

Self-Interference Cancellation (SIC)

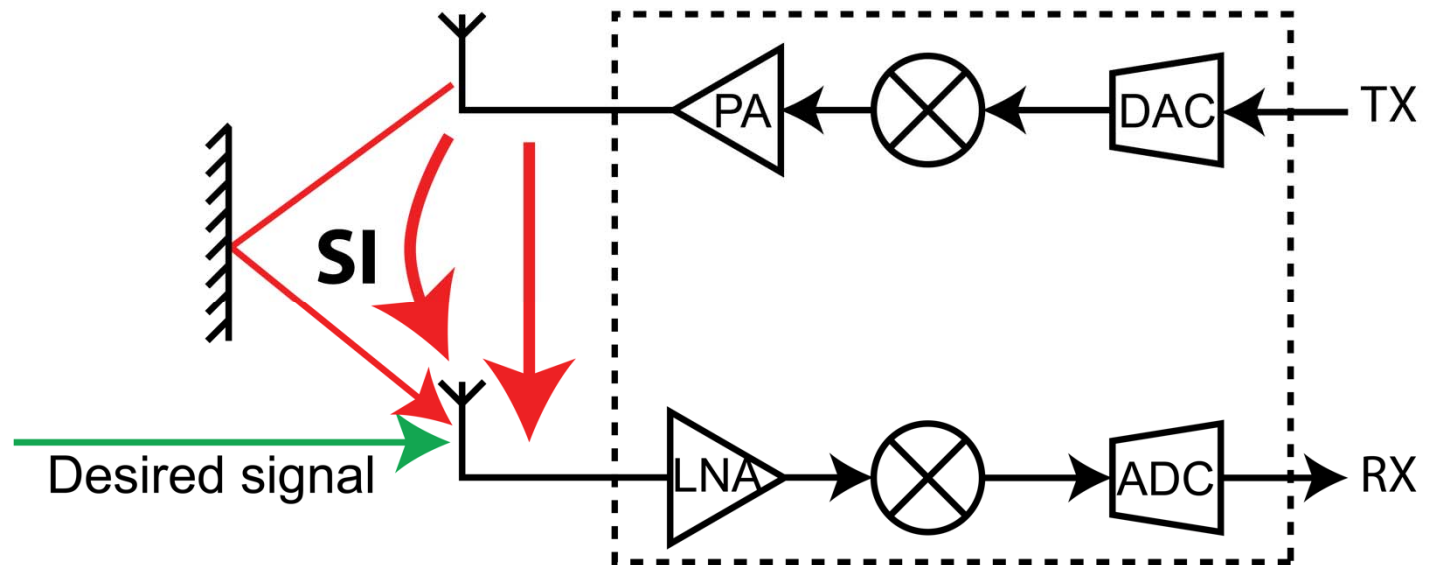


Handheld device → varying antenna isolation

→ e.g. 20 dB worst-case *isolation*

→ $90 - 20 = 70$ dB *cancellation* required

Self-Interference Cancellation

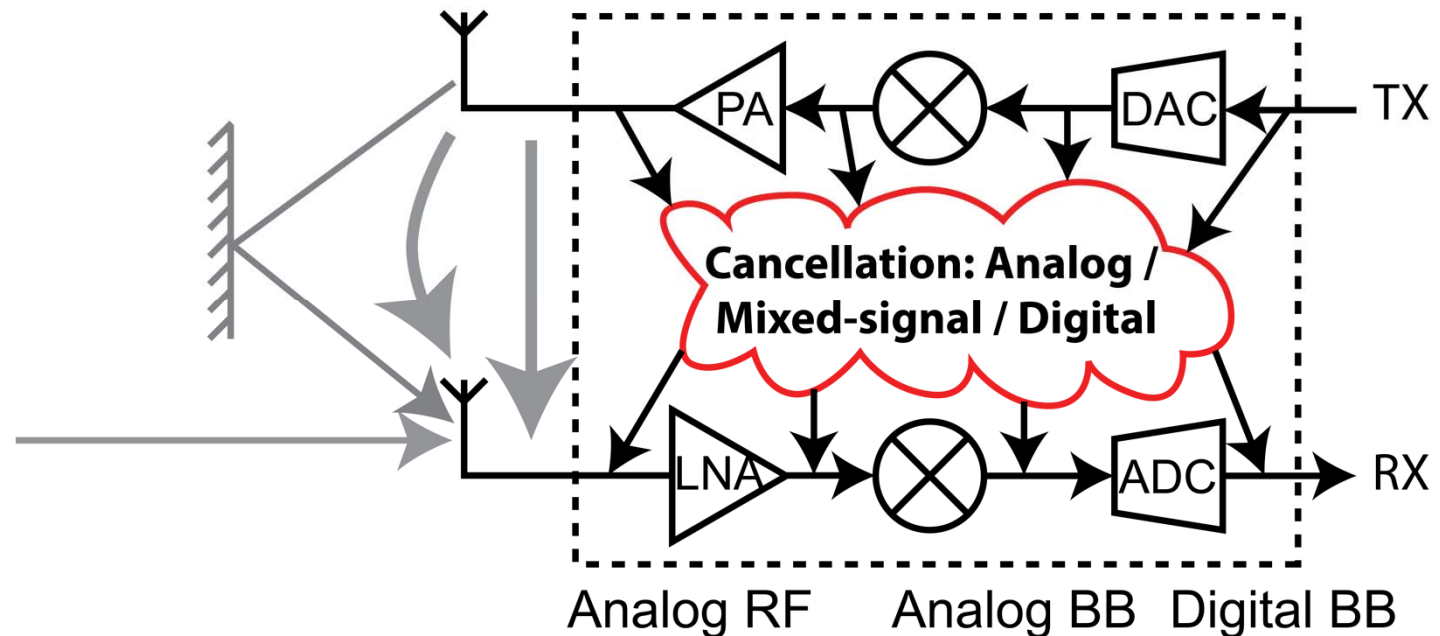


Handheld device → varying antenna isolation

→ e.g. 20 dB worst-case *isolation*


→ $90 - 20 = 70$ dB *cancellation* required

Digital-only SI-Cancellation

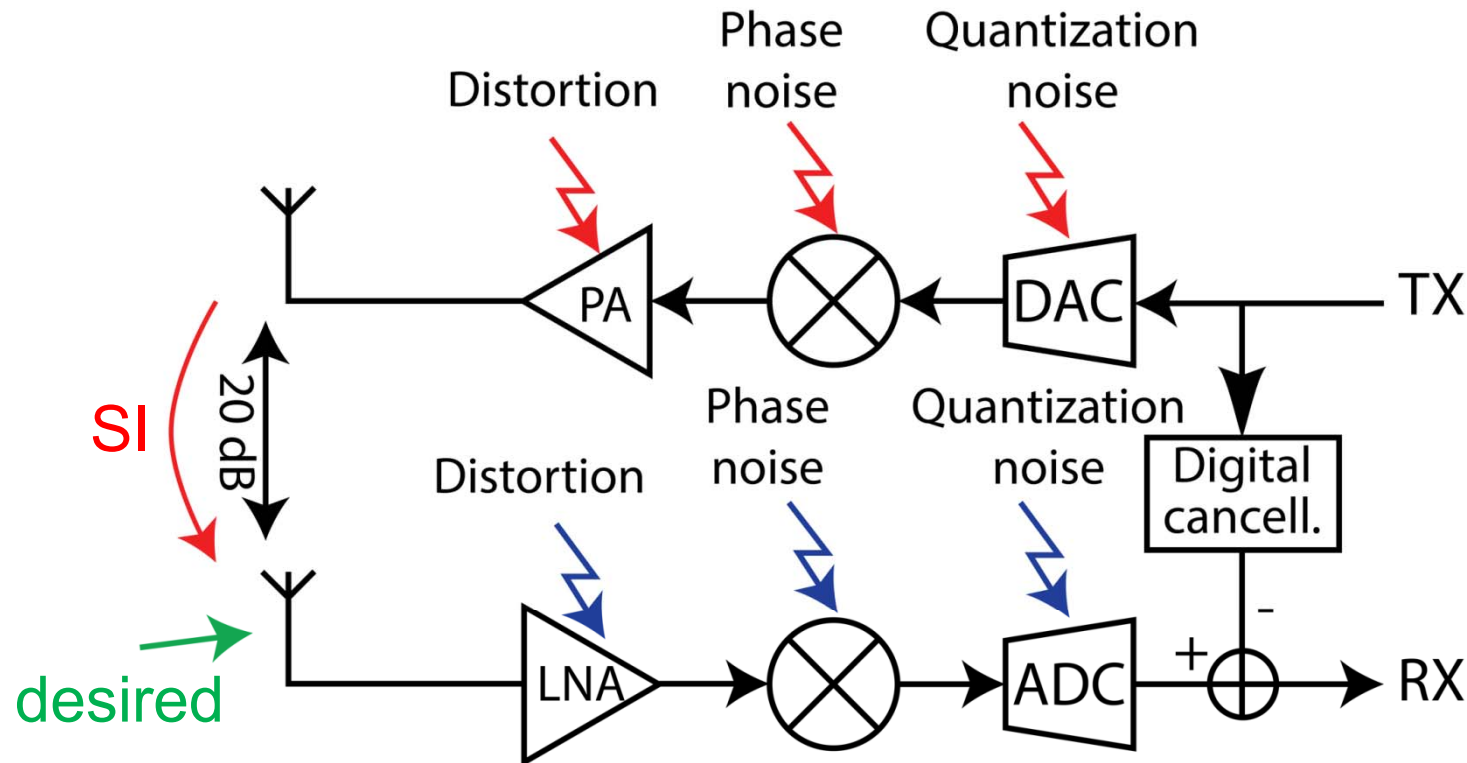


Deterministic components → cancel in digital
Noisy components must be 90dB down before digital!!

Digital-only SI-Cancellation

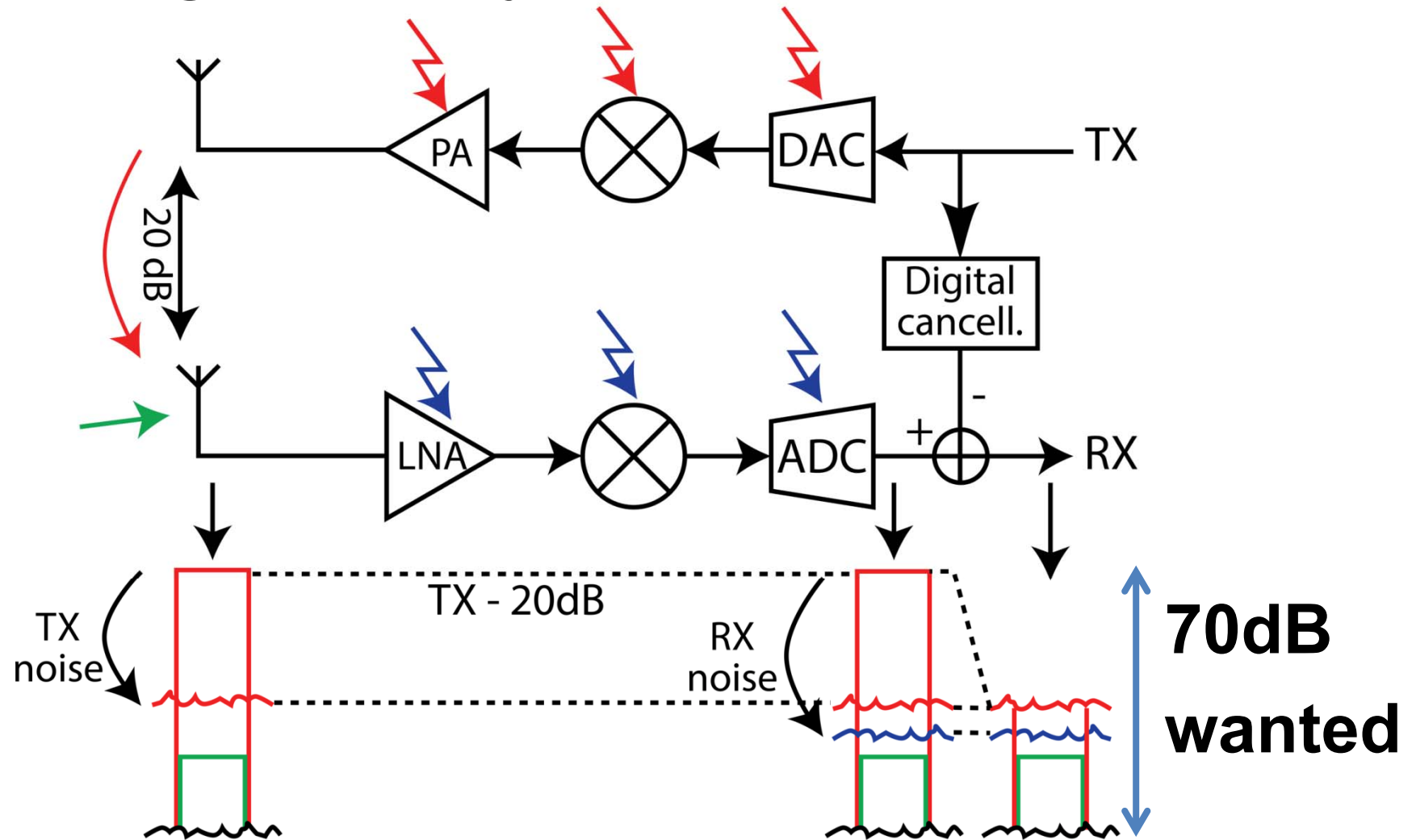


70dB TX EVM & RX dynamic range required

RF + digital SI-Cancellation

 


40-50 dB TX EVM & RX dynamic range required

RF + Digital SI-Cancellation

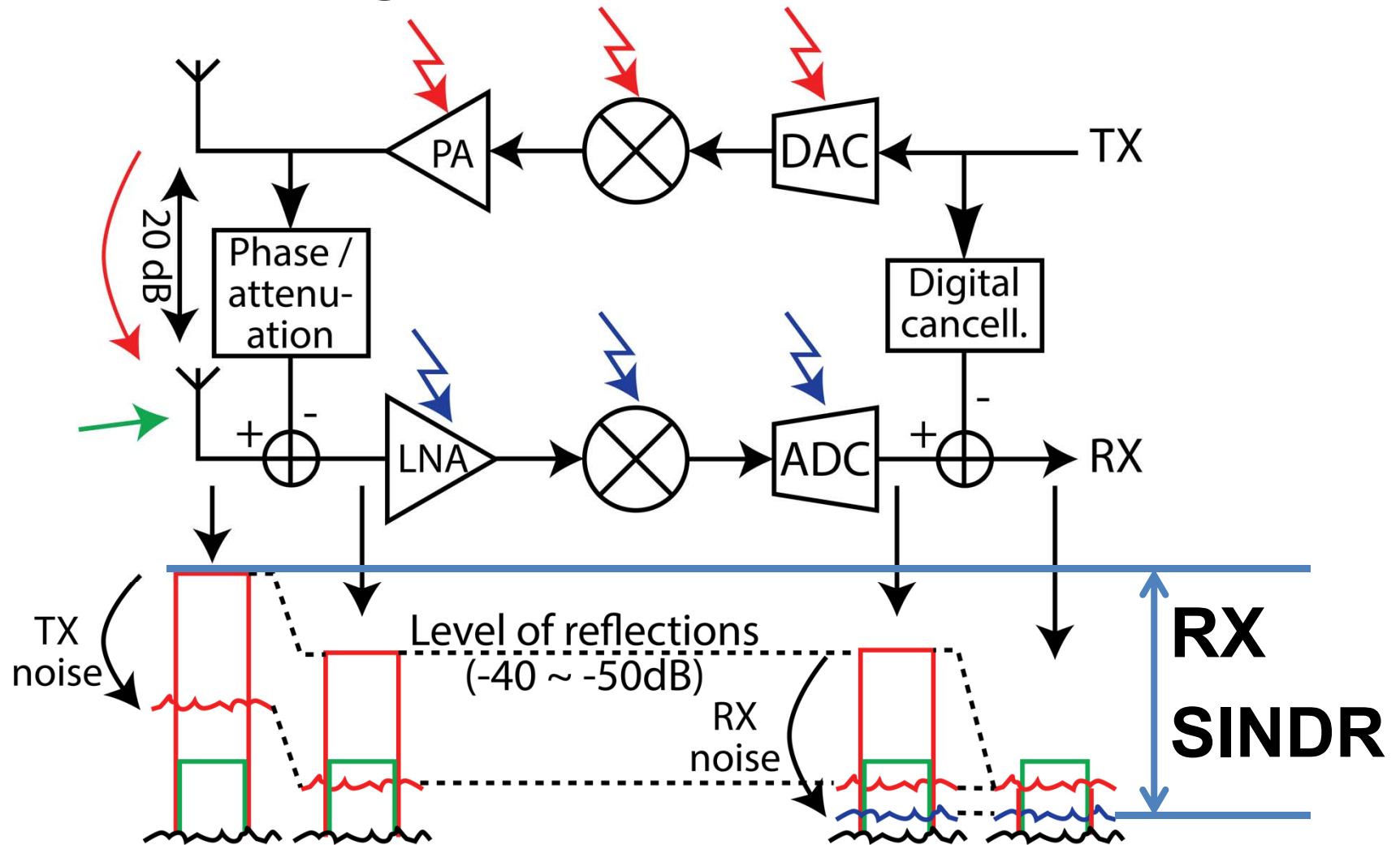


Self-interference-to-Noise-and-Distortion ratio

RF + Digital SI-Cancellation

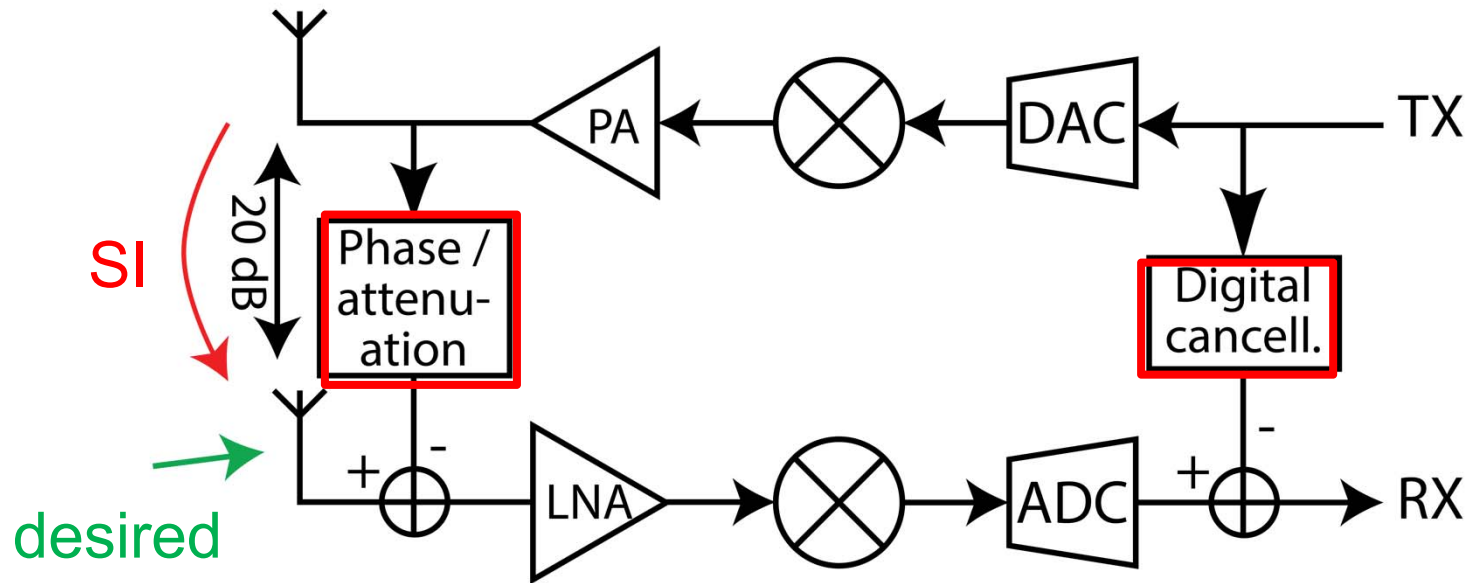


RF + digital SI-Cancellation

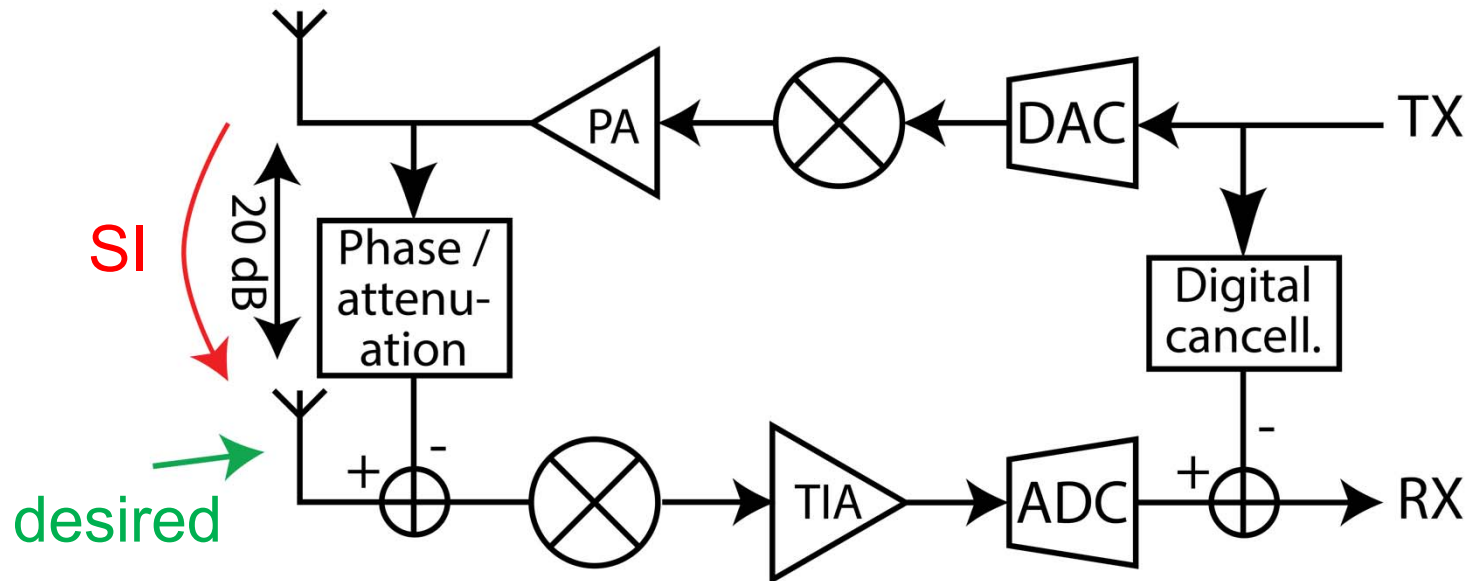


Mixer-first architecture for good linearity

Cross-domain cancellation

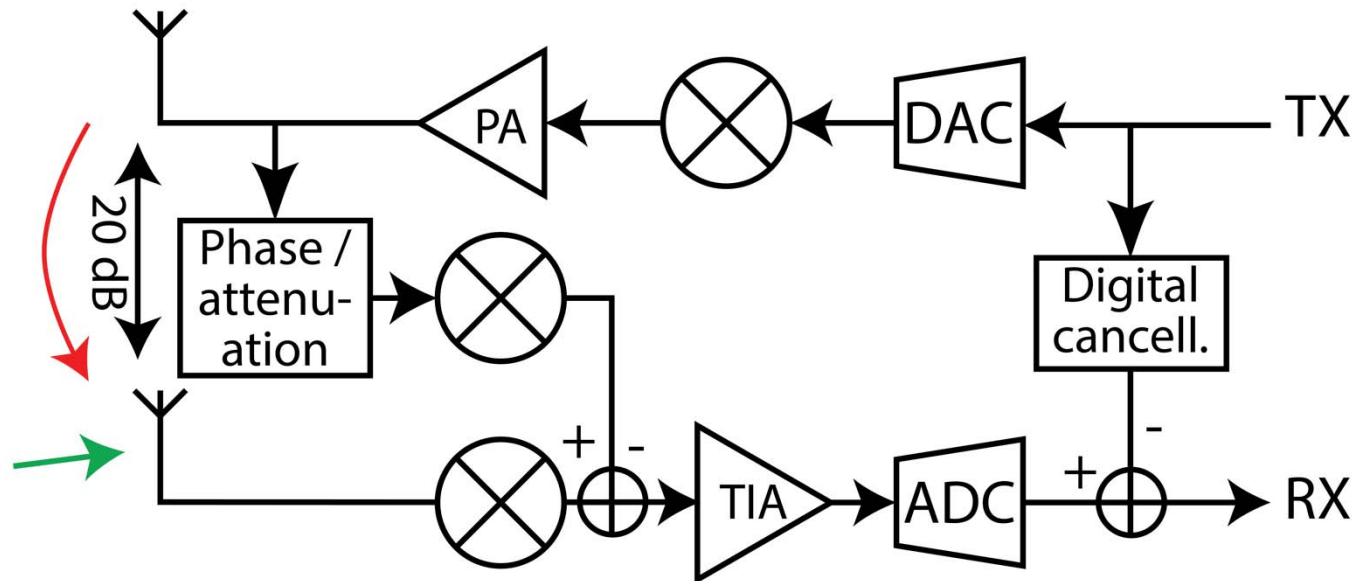


Cancellation TX RF \rightarrow RX analog BB

Cross-domain cancellation

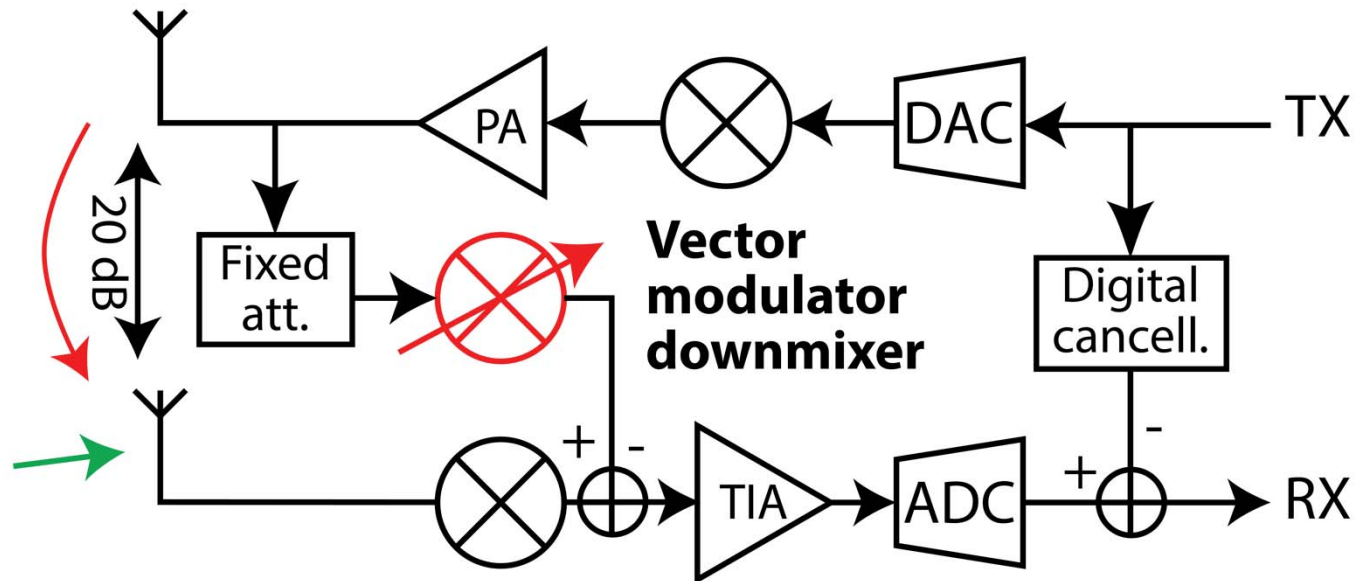


Combine phase, attenuation & downmixing

Prototype front-end

 


Short-range, low-power full-duplex
High integration potential

Prototype front-end

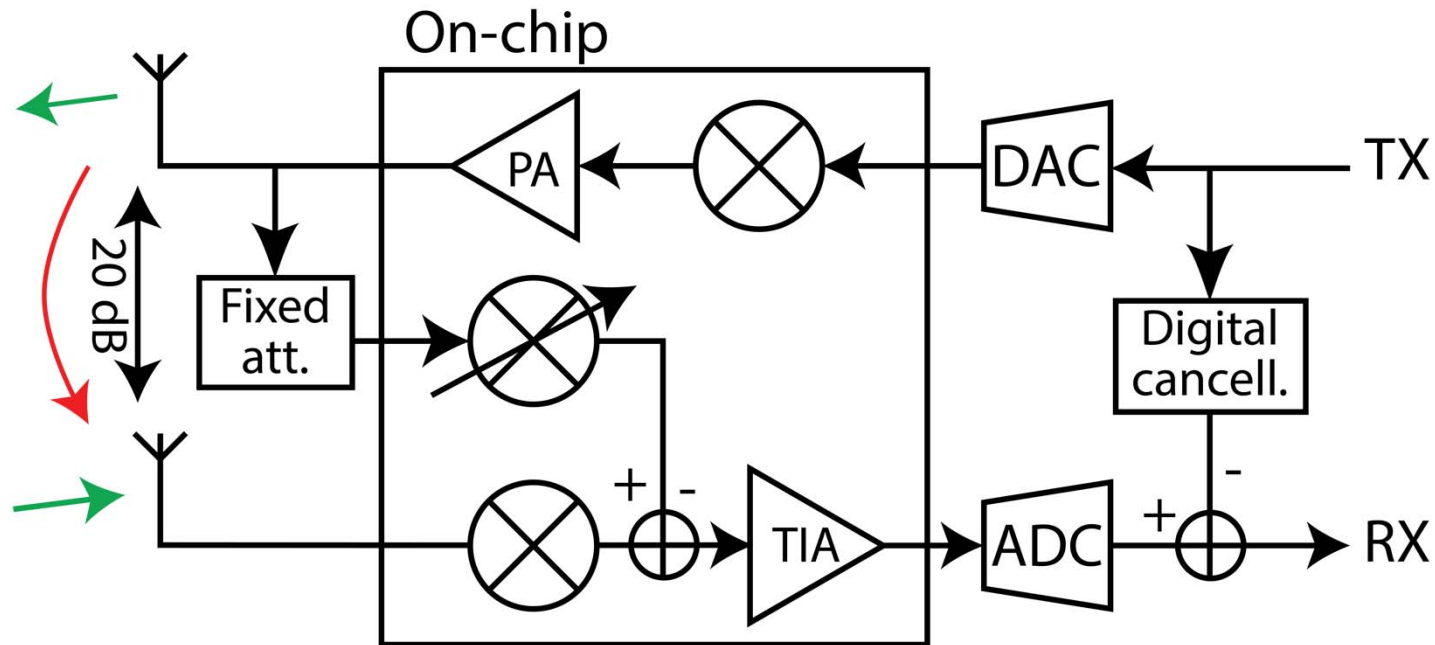

- VM \rightarrow robust cancellation for changing near-field
- Attenuator sets VM range to worst-case SI

Prototype front-end

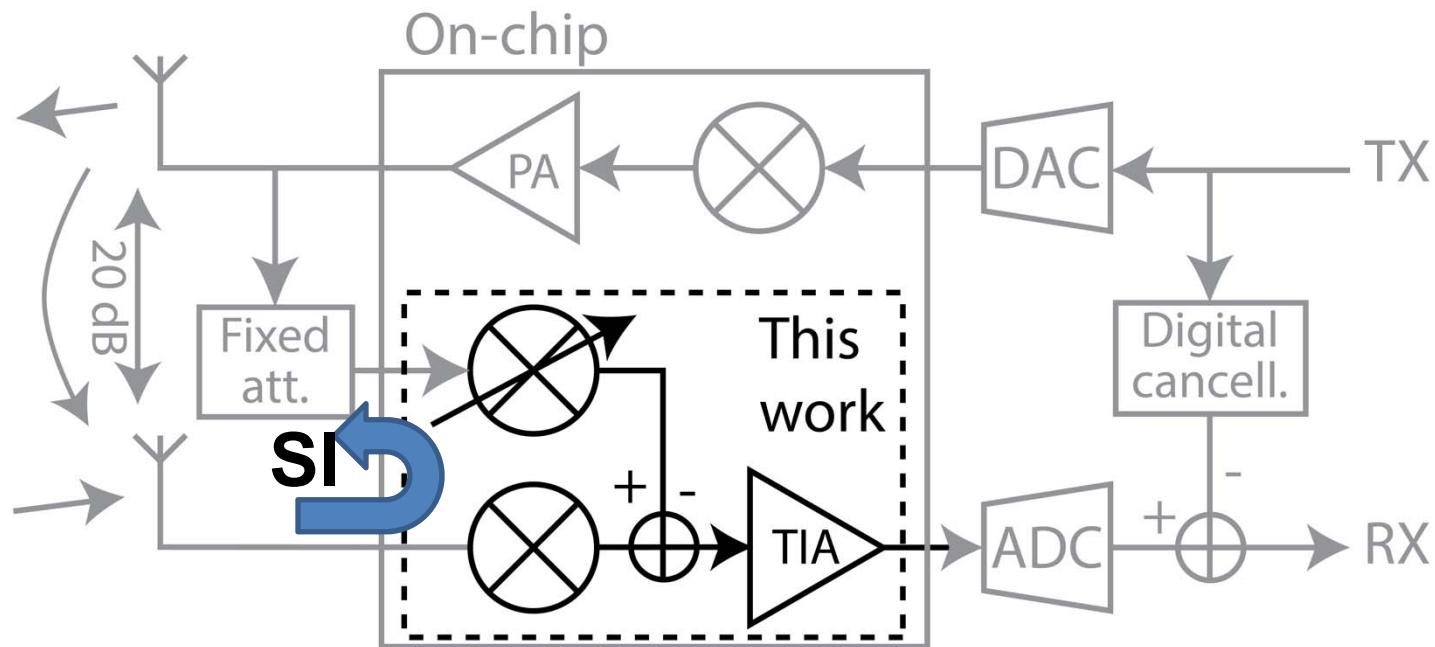


Mixers process full SI power:

Linearity crucial for high SINDR → Passive mixers


TIA and ADC after cancellation: relaxed

Main RX

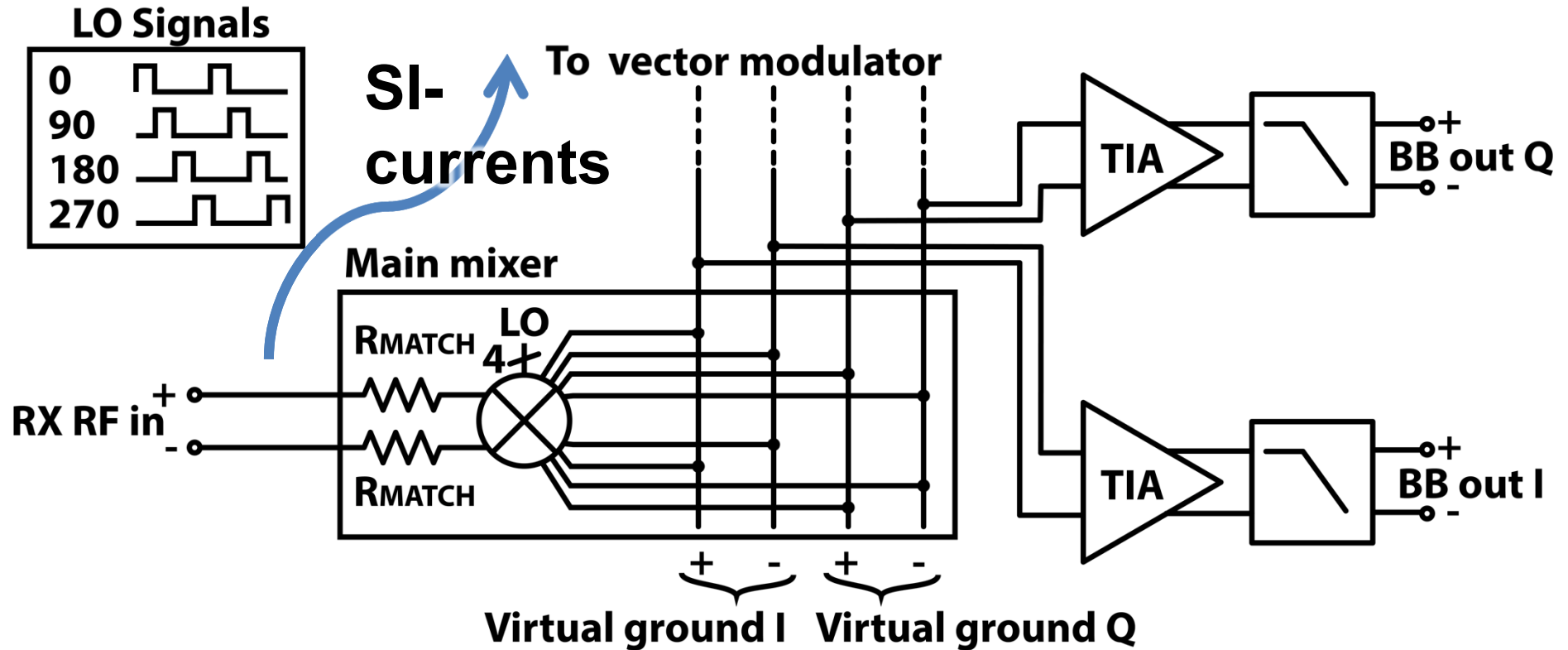

Switched resistor to virtual ground

Vector modulator

 

SI-currents diverted through passive networks


Vector modulator

- VM = sliced main mixer + static phase rotator

- Principle:

1 slice:

- 2x2 grid
- 4 points (I / Q)

 

Vector modulator


- VM = sliced main mixer + static phase rotator

- Principle:

3 slices: (2 MSB + 1 LSB)


- 4x4 grid
- 16 points

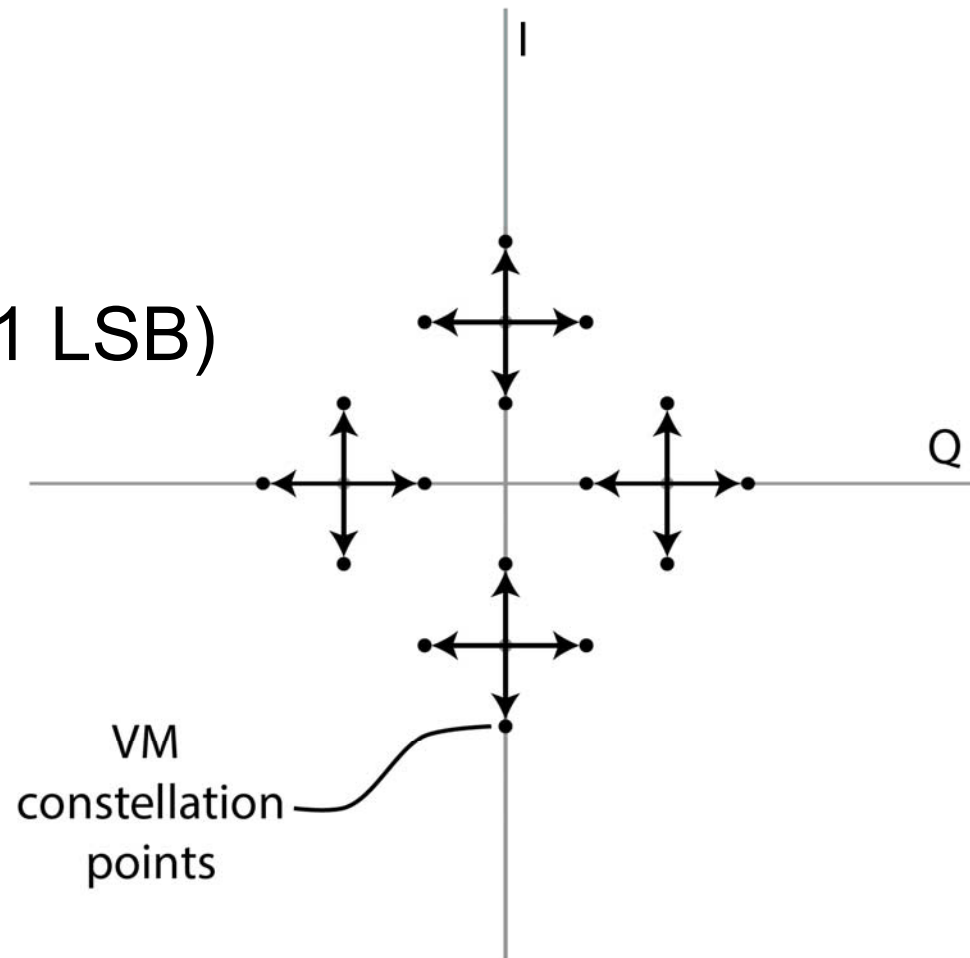[Soer, ISSCC'14]
(sliced Gm-mixer
instead of sliced-R)




Vector modulator

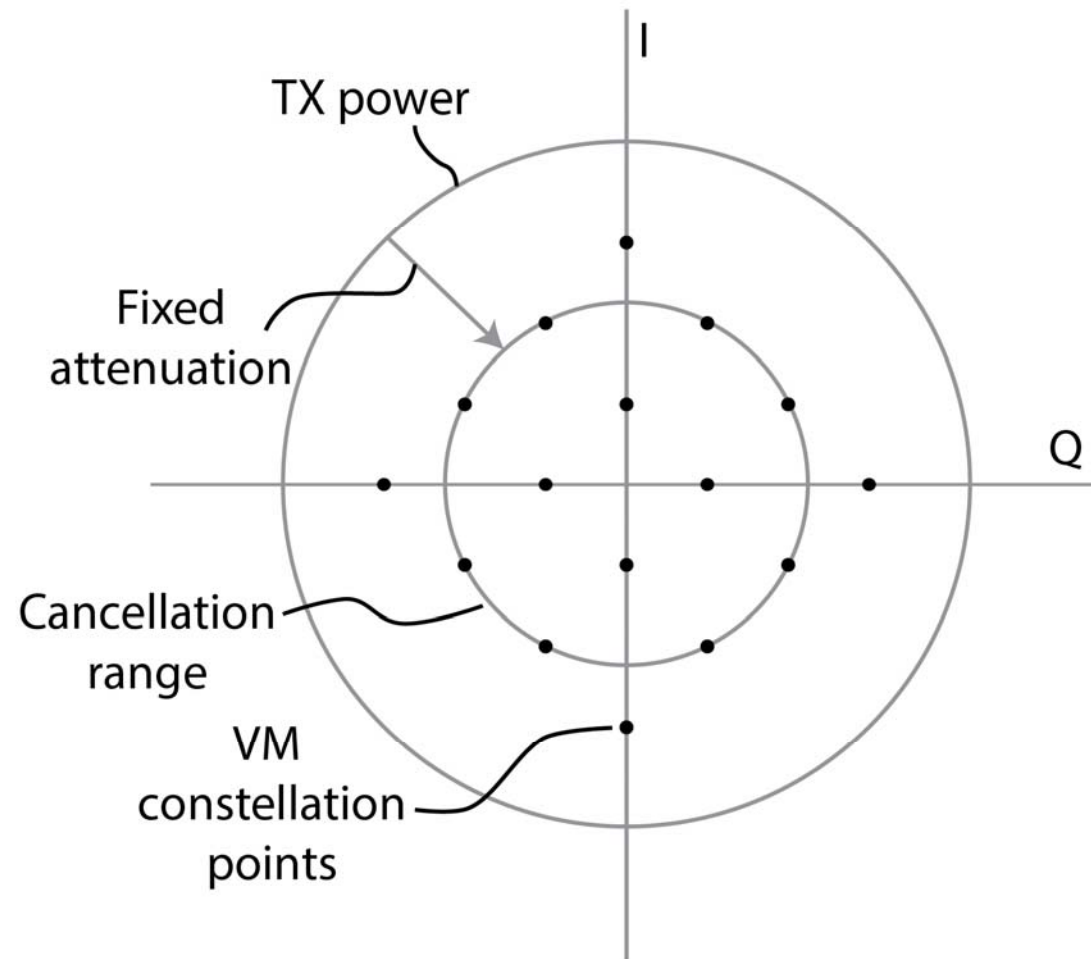- VM = sliced main mixer + static phase rotator
- Principle:



Vector modulator

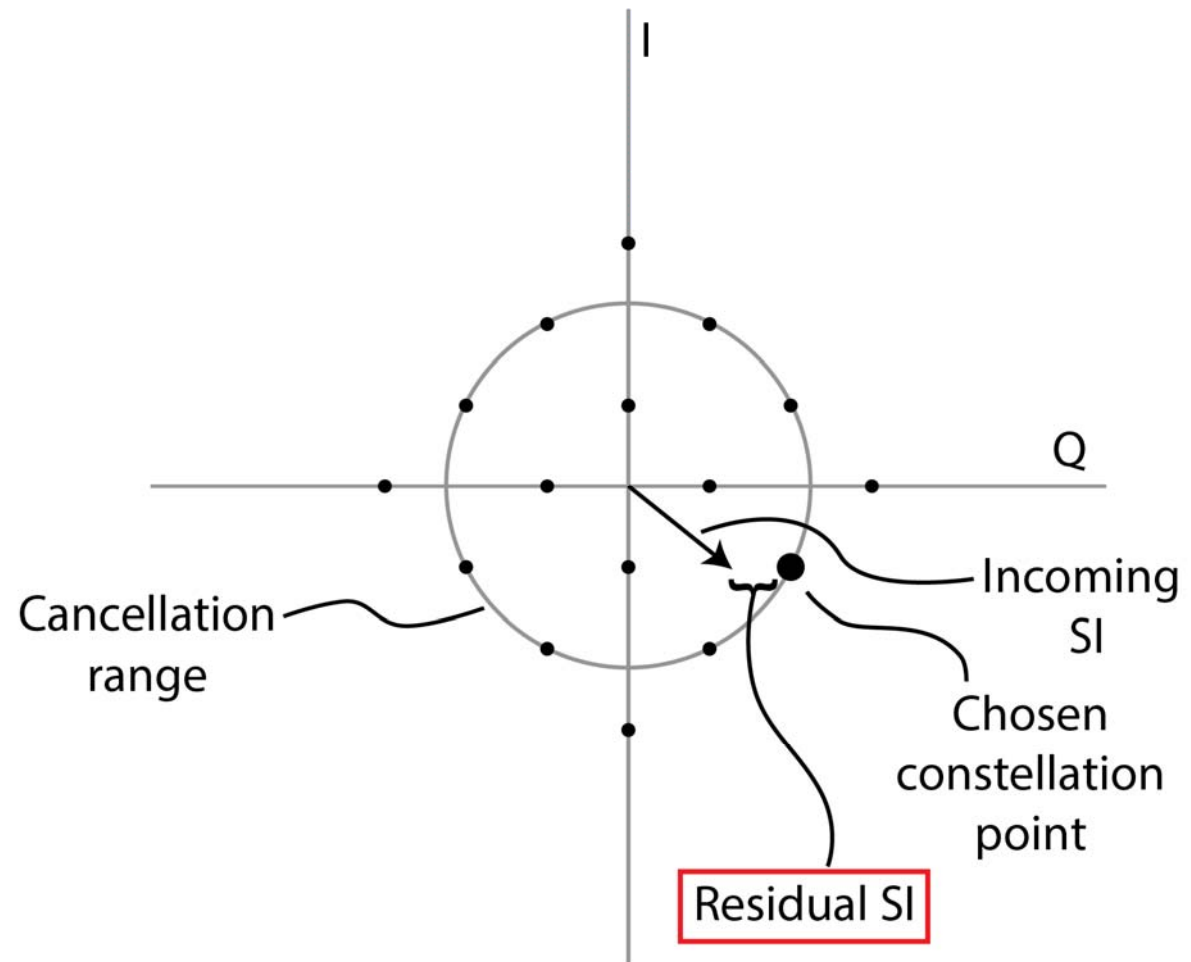- VM = sliced main mixer + static phase rotator
- Principle:




Vector modulator

- VM = sliced main mixer + static phase rotator


31 slices: (“5 bits”)

- 32x32 grid
- 1024 points
 - 28.5 dB worst-case cancellation

Single VM slice

 

Chip photograph

 

65nm CMOS

1.2V supply

1.4x1.4mm


Measured: Cancellation

- 20 tones in 16.25 MHz BW @ 2.5 GHz (WLAN-like)
- Emulated SI channel: arbitrary phase & amplitude
- On-chip VM finds best cancellation point
 - Search algorithm: power minimization


Measured: Cancellation

- 20 tones in 16.25 MHz BW @ 2.5 GHz (WLAN-like)
- Emulated SI channel: arbitrary phase & amplitude
- On-chip VM finds best cancellation point
 - Search algorithm: power minimization


Emulated SI-channel

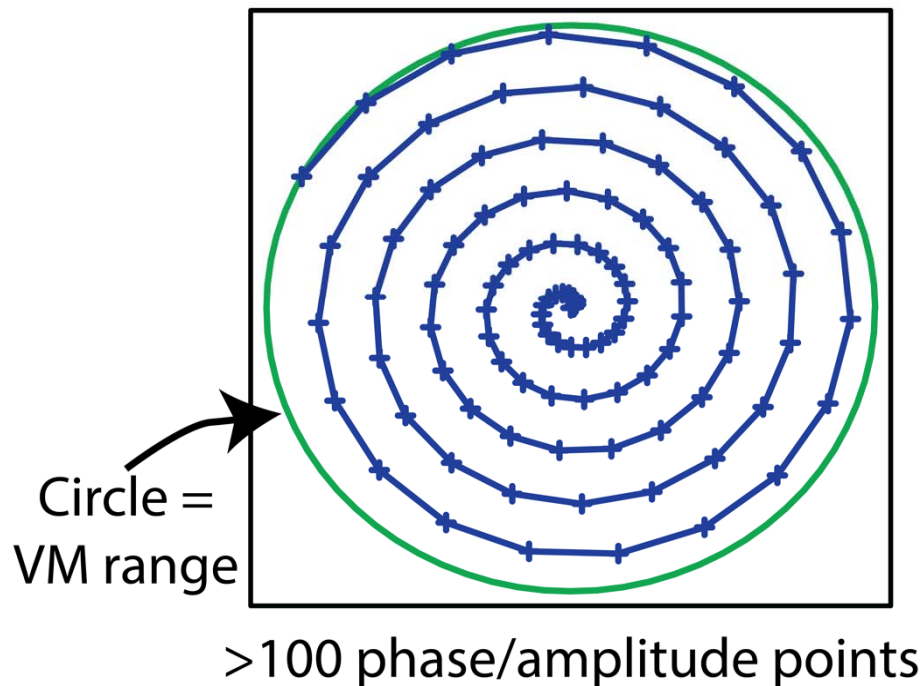

On-chip VM setting

 


Measured: Cancellation

 

>27dB cancellation for all points


Measured IM3 without SIC

- 2-tone self-interferer
- 2.5 GHz

 


Resulting SINDR without SIC

- 2-tone self-interferer
- 2.5 GHz

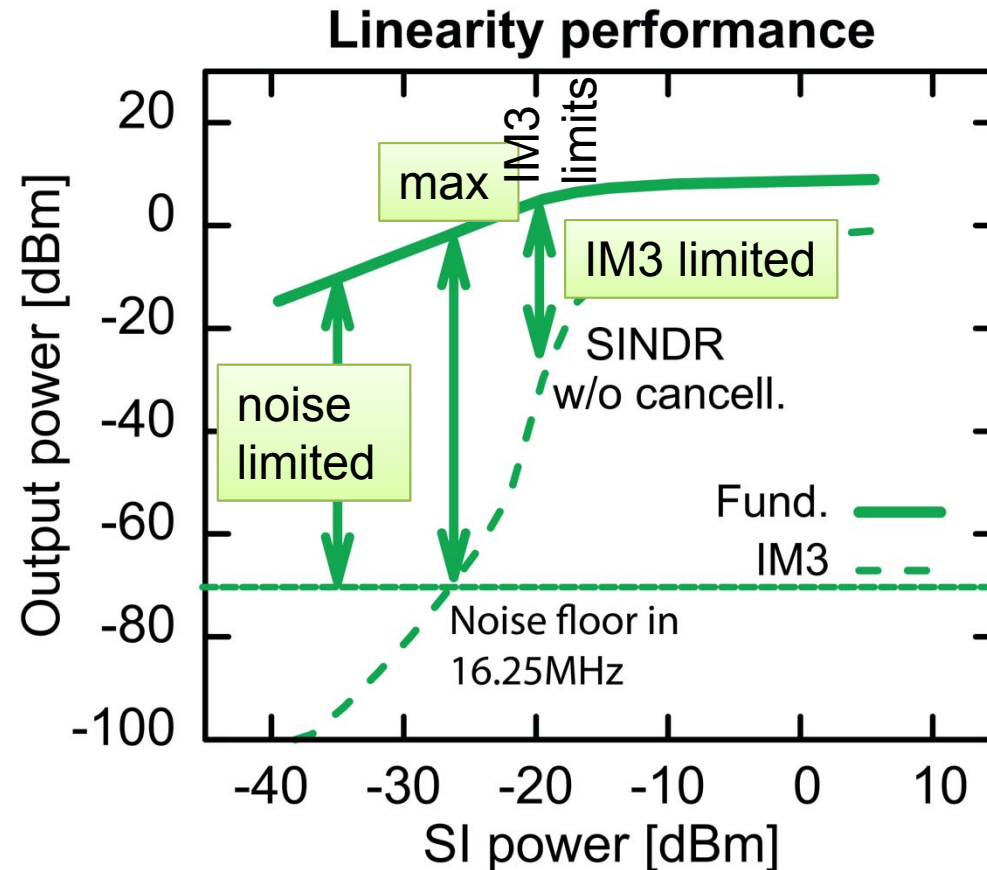


Measured IM3 with SIC

- 2-tone self-interferer
- 2.5 GHz

 


Resulting SINDR with SIC

- 2-tone self-interferer
- 2.5 GHz

 

SINDR Comparison


- In 16.25 MHz BW

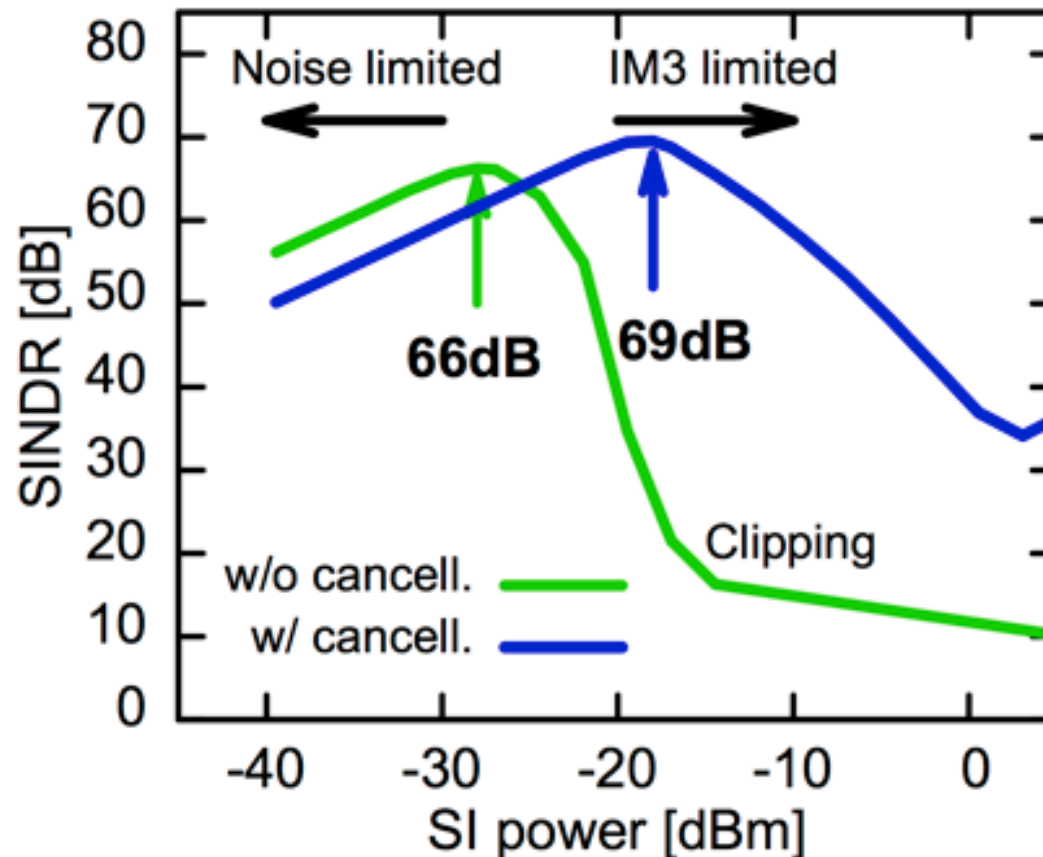

3dB higher SINDR @ 10dB higher SI

Derived SINDR


- In 16.25 MHz BW

 

Stronger SI:
Smooth
degradation
of SINDR,
no clipping

3dB higher SINDR @ 10dB higher SI

Conversion gain under SI

 

Desired signal only compressed at >0 dBm SI

Linearity & cancellation: Summary

Assuming 20 dB antenna-isolation

	w/o cancell.	w/ cancell.
Maximum link budget (SINDR + isolation)	66+20 = 86dB	69+20 = 89dB

Linearity & cancellation: Summary

Assuming 20 dB antenna-isolation

	w/o cancell.	w/ cancell.
Maximum link budget (SINDR + isolation)	86 dB <small>20dB isol.</small>	89 dB <small>20dB isol. + 27dB canc.</small>
Digital cancellation requirement (SINDR – cancellation)	66 dB	$69 - 27$ = 42 dB

ADC and TX EVM requirements:
reduced to feasible levels

Linearity & cancellation: Summary

Assuming 20 dB antenna-isolation

	w/o cancell.	w/ cancell.
Maximum link budget (SINDR + isolation)	86 dB	89 dB
Digital cancellation requirement (SINDR – cancellation)	66 dB	42 dB
TX power @ max. link budget (SI + isolation)	$-28+20 =$ -8 dBm	$-18+20 =$ 2 dBm


Linearity & cancellation: Summary

Assuming 20 dB antenna-isolation

	w/o cancell.	w/ cancell.
Maximum link budget (SINDR + isolation)	86 dB	89 dB
Digital cancellation requirement (SINDR – cancellation)	66 dB	42 dB
TX power @ max. link budget (SI + isolation)	-8 dBm	2 dBm

Short-range full-duplex achievable

Broadband RX performance

 

Frequency-flexible operation & cancellation

Performance summary

	Molnar, RFIC2014	This work
Topology	Duplexer LNA's	SI-cancelling VM
Technology	65nm CMOS 1.2/2.5V	65nm CMOS 1.2V
Operating freq.	0.1 - 1.5 GHz	0.15 - 3.5 GHz
Power cons.	43-56mW	23-56mW
Noise figure	5-8dB	10.3-12.3dB (HD: 6.3)
Baseband BW	-	24 MHz (2x12)
TX/RX isolation	33dB	27dB
SINDR in 16.25MHz	57 dB peak @ -38 dBm SI*	69.5 dB peak @ -18 dBm SI
Effective in- band IIP3	-7.2 dBm*	+19 dBm

No antenna isolation assumed for fair comparison

* Derived from reported IIP3's and NF

Conclusions

- Cancel strong interference by Passive switch-R-C
- Notch N-path filter: rejection at clock frequency
- SI-cancelling receiver in 65nm CMOS:
 - Phase / amplitude / downmixing: Vector Modulator
 - Frequency-flexible operation & cancellation
 - Mixer-first → Divert SI by passive networks
→ Good in-band linearity → high SINDR
 - Relaxed ADC and TX EVM requirements
- Total ~89 dB link budget potential in 16.25 MHz
 - Enables low-power, short-range full-duplex wireless